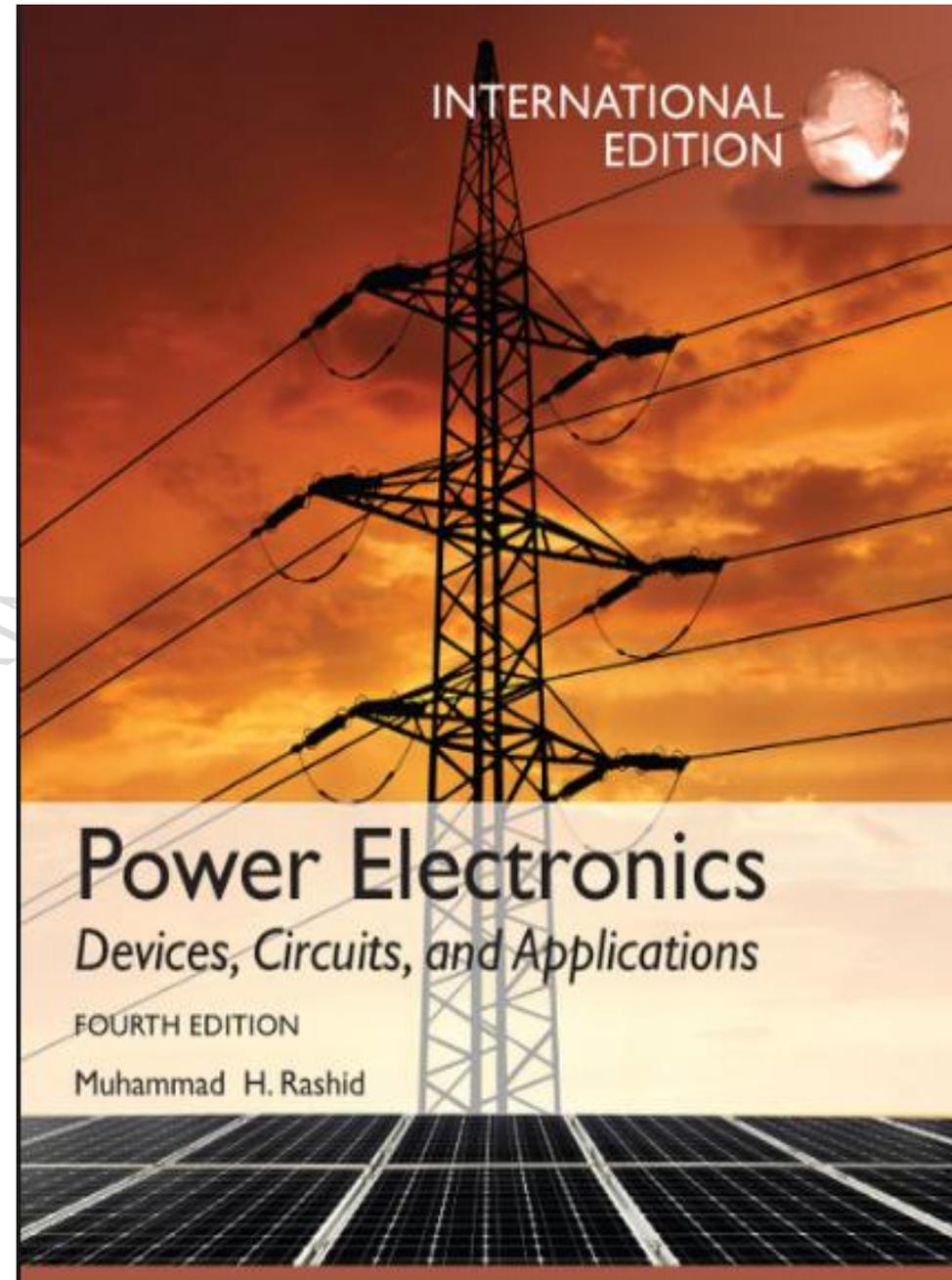


University of Technology
Laser and Optoelectronic Engineering
Department
Power Electronics/2018-2019)
For the third years (Laser Engineering)

Prepared by: Lec. Dr. Mothana Amaar Hassan
Laser and Optoelectronic Engineering
Department



Ref: Power Electronics 4th edition/ Muhammed H. Rashid

Lecture No.1

INTRODUCTION TO POWER ELECTRONICS

Definition

- Power electronics refers to control and conversion of electrical power by power semiconductor devices wherein these devices operate as switches.
- Advent of silicon-controlled rectifiers, abbreviated as SCRs, led to the development of a new area of application called the power electronics.
- Prior to the introduction of SCRs, mercury-arc rectifiers were used for controlling electrical power, but such rectifier circuits were part of industrial electronics and the scope for applications of mercury-arc rectifiers was limited.
- Once the SCRs were available, the application area spread to many fields such as drives, power supplies, aviation electronics & high frequency inverters.

Main Task of Power Electronics

- Power electronics has applications that span the whole field of electrical power systems, with the power range of these applications extending from a few VA/Watts to several MVA / MW.
- The main task of power electronics is to control and convert electrical power from one form to another.
- The four main forms of conversion are:
 - **Rectification referring to conversion of AC voltage to DC voltage,**
 - **DC-to-AC conversion,**
 - **DC-to DC conversion,**
 - **AC-to-AC conversion**

- "Electronic power converter" is the term that is used to refer to a power electronic circuit that converts voltage and current from one form to another.

These converters can be classified as:

- Rectifier converting an ac voltage to a dc voltage,
- Inverter converting a dc voltage to an ac voltage,
- Chopper or a switch-mode power supply that converts a dc voltage to another dc voltage, and
- Cycloconverter converts an ac voltage to another ac voltage.

Rectification

- Rectifiers can be classified as uncontrolled and controlled rectifiers, and the controlled rectifiers can be further divided into semi-controlled and fully controlled rectifiers.
- Uncontrolled rectifier circuits are built with diodes, and fully controlled rectifier circuits are built with SCRs. Both diodes and SCRs are used in semi-controlled rectifier circuits.
- There are several rectifier configurations. The popular rectifier configurations are listed below.
 - Single-phase half wave rectifier,
 - Single-phase full wave rectifier,
 - Single-phase half wave controlled rectifier,
 - Single-phase semi-controlled full wave rectifier,
 - Single-phase fully controlled full wave rectifier,
 - Three-phase half wave rectifier,
 - Three-phase bridge rectifier,
 - Three-phase half wave controlled rectifier,
 - Three-phase semi-controlled bridge rectifier
 - Three-phase fully controlled bridge rectifier
- Power rating of a single-phase rectifier tends to be lower than 10 kW. Three-phase bridge rectifiers are used for delivering higher power output, up to 500 kW at 500 V dc or even more.
- There are many applications for rectifiers. Some of them are:
 - Variable speed dc drives,
 - Battery chargers,
 - DC power supplies and Power supply for a specific application like electroplating

DC-to-AC Conversion

- The converter that changes a dc voltage to an alternating voltage is called an inverter.
- Earlier inverters were built with SCRs.
- Since the circuitry required turning the SCR off tends to be complex, other power semiconductor devices such as bipolar junction transistors, power MOSFETs, insulated gate bipolar transistors (IGBT) and MOS- controlled thyristors (MCTs) are used nowadays.
- Some of the applications of an inverter are listed below:
 - Emergency lighting systems,
 - AC variable speed drives,

- Uninterrupted power supplies,
- Frequency converters

DC-to-DC Conversion

- A SCR, power BJT or a power MOSFET is normally used in such a converter and this converter is called a switch-mode power supply.
- A switch-mode power supply can be of one of the types listed below:
 - Step-down switch-mode power supply,
 - Step-up switch-mode power supply,
 - Fly-back converter,
 - Resonant converter
- The typical applications for a switch-mode power supply or a chopper are:
 - DC drive
 - Battery charger
 - DC power supply

AC-to-AC Conversion

- A cycloconverter converts an ac voltage, such as the mains supply, to another ac voltage.
- The amplitude and the frequency of input voltage to a cycloconverter tend to be fixed values, whereas both the amplitude and the frequency of output voltage of a cycloconverter tend to be variable.
- A typical application of a cycloconverter is to use it for controlling the speed of AC traction motor and most of these cycloconverters have a high power output, of the order a few megawatts and SCRs are used in these circuits.


Power electronic devices (part I)

1. The power diode


Diode Approximations

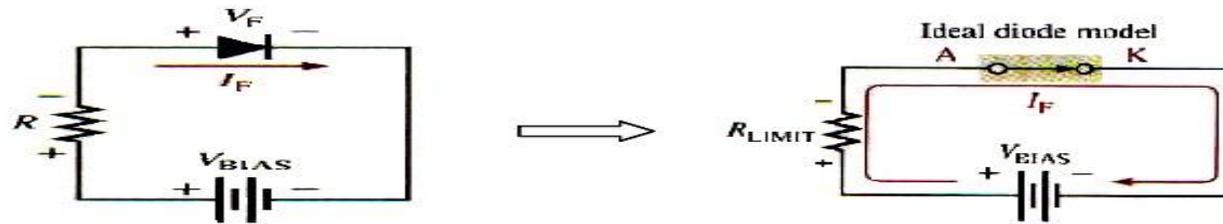i. The Ideal Model


- Think it as switch
- When forward biased, act as a closed (ON) switch
- When reverse biased, act as open (off) switch



Ideal diode model for forward bias

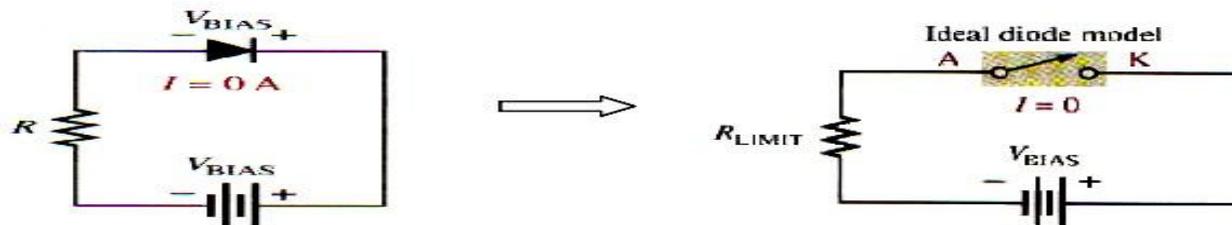

Ideal diode model for reverse bias



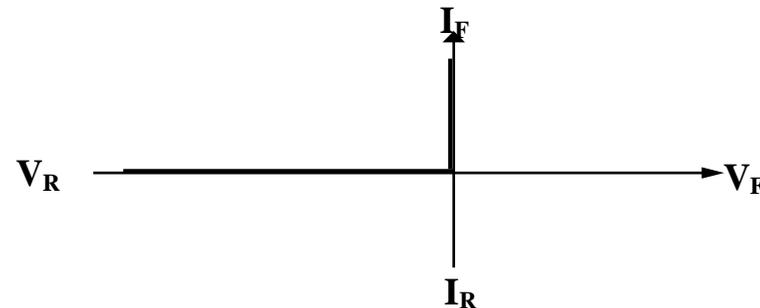


Ideal Characteristic curve (blue) for Ideal model

- This model neglects the effect of the barrier potential, the internal resistance, and other parameters.

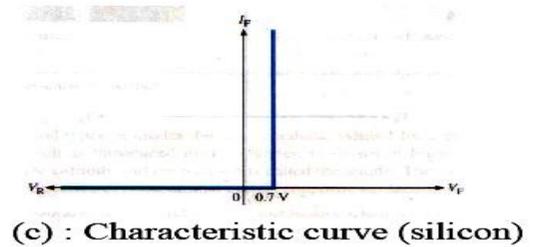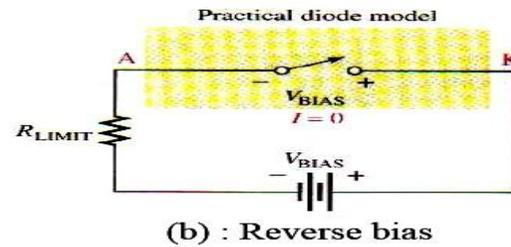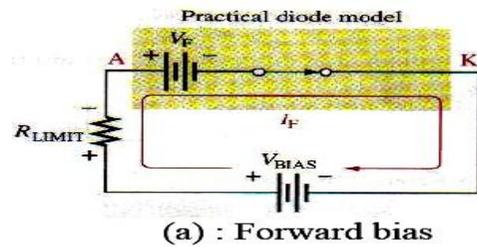ii. The Barrier Potential Model



- The forward biased diode is represented as a closed switch in series with a small ‘battery’ equal to the barrier potential V_B (0.7 V for Si and 0.3 V for Ge)
- The positive end of the equivalent battery is toward the anode.
- This barrier potential cannot be measured by using a multimeter, but it has the effect of a battery when forward bias is applied.
- The reverse biased diode is represented by an open switch, because barrier potential does not affect reverse bias.




The practical model of a diode

The Complete Diode Model

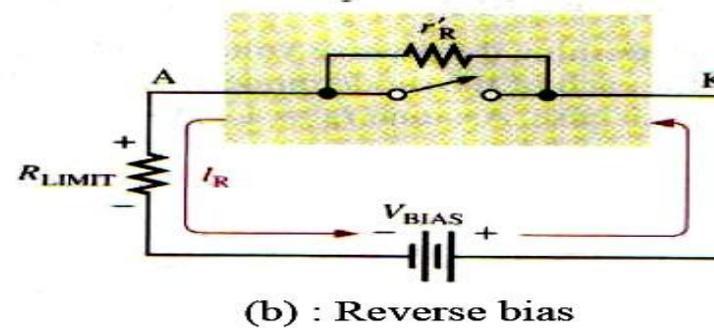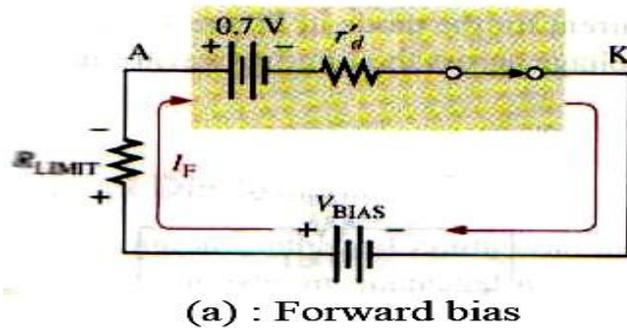- More accurate
- The forward biased diode model with both the barrier potential and low forward (bulk) resistance (r'_d)



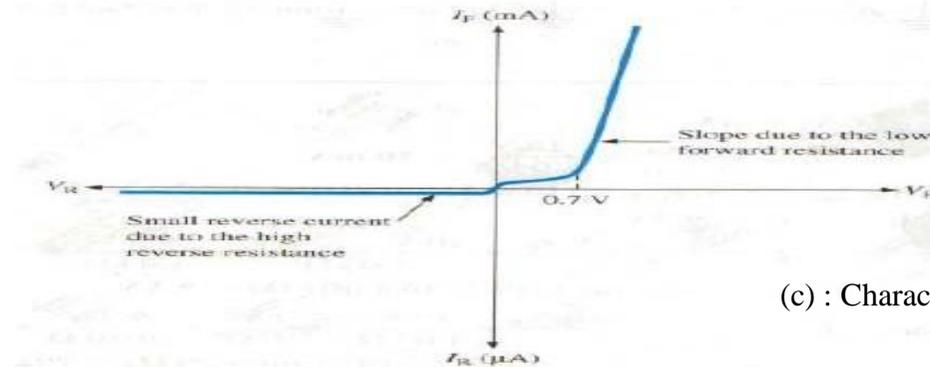

(c) : Characteristic curve (silicon)

Diode Characteristics

- A power diode is a two terminal pn – junction device.
- The magnitude of this voltage drop depends on:
 - a) on the manufacturing process
 - b) junction temperature
- When the cathode potential is positive with respect to the anode:
 - ⇒ The diode is said to be reverse biased
 - ⇒ A small reverse current (also known as leakage current) in the range of micro or miliampere, flows through it.
 - ⇒ It increases slowly in magnitude with the reverse voltage until the avalanche or zener voltage is reached.
- The $v - I$ characteristics shown above can be expressed by an equation known as ‘Schockley diode equation’ and it is given under dc steady state operation by:

$$I_D = I_S \left(e^{V_D / nV_T} - 1 \right)$$

- Where:

I_D = Current through the diode, A

V_D = Diode voltage (forward voltage)

I_S = Leakage current (or reverse saturation). n = emission coefficient

V_T = Thermal Voltage

$$V_T = \frac{kT}{q}$$

q = electron charge : 1.6022×10^{-19} C T = absolute temperature in Kelvin

k = Boltzman's constant : 1.3806×10^{-23} J / K

• The diode characteristics can be divided into three region:

1. Forward – biased region, where $V_D > 0$
2. Reverse – biased region, where $V_D < 0$
3. Breakdown region, where $V_D < -V_{BR}$

Forward – biased region

- $V_D > 0$
- Diode current I_D very small if V_D is less than a specific value V_T (0.7V)
- Diode conducts fully if V_D is higher than this value V_T , which is referred to as the threshold voltage or the turn-on voltage
- The threshold voltage is a voltage at which the diode conducts fully.

Reverse – biased region

- $V_D < 0$
- If V_D is negative and $|V_D| \gg V_T$, which occurs for $V_D < -0.1$, the exponential term in Shockley equation becomes negligibly small compared to unity and the diode current I_D becomes:

$$I_D = I_S (e^{V_D / nV_T} - 1) \cong -I_S$$

Breakdown region

- Reverse voltage is high.
- Magnitude of reverse voltage exceeds a specified voltage known as the breakdown voltage, V_{BR}
- I_R increases rapidly with a small change in reverse voltage beyond V_{BR} .
- The operation in this region will not be destructive provided that the power dissipation is within a 'safe level' that is specified in the manufacture's data sheet.
- But it has to limit I_R in order to limit the power dissipation within a permissible value


Home work :

The forward voltage drop of a power diode is $V_D = 1.2$ V at $I_D = 300$

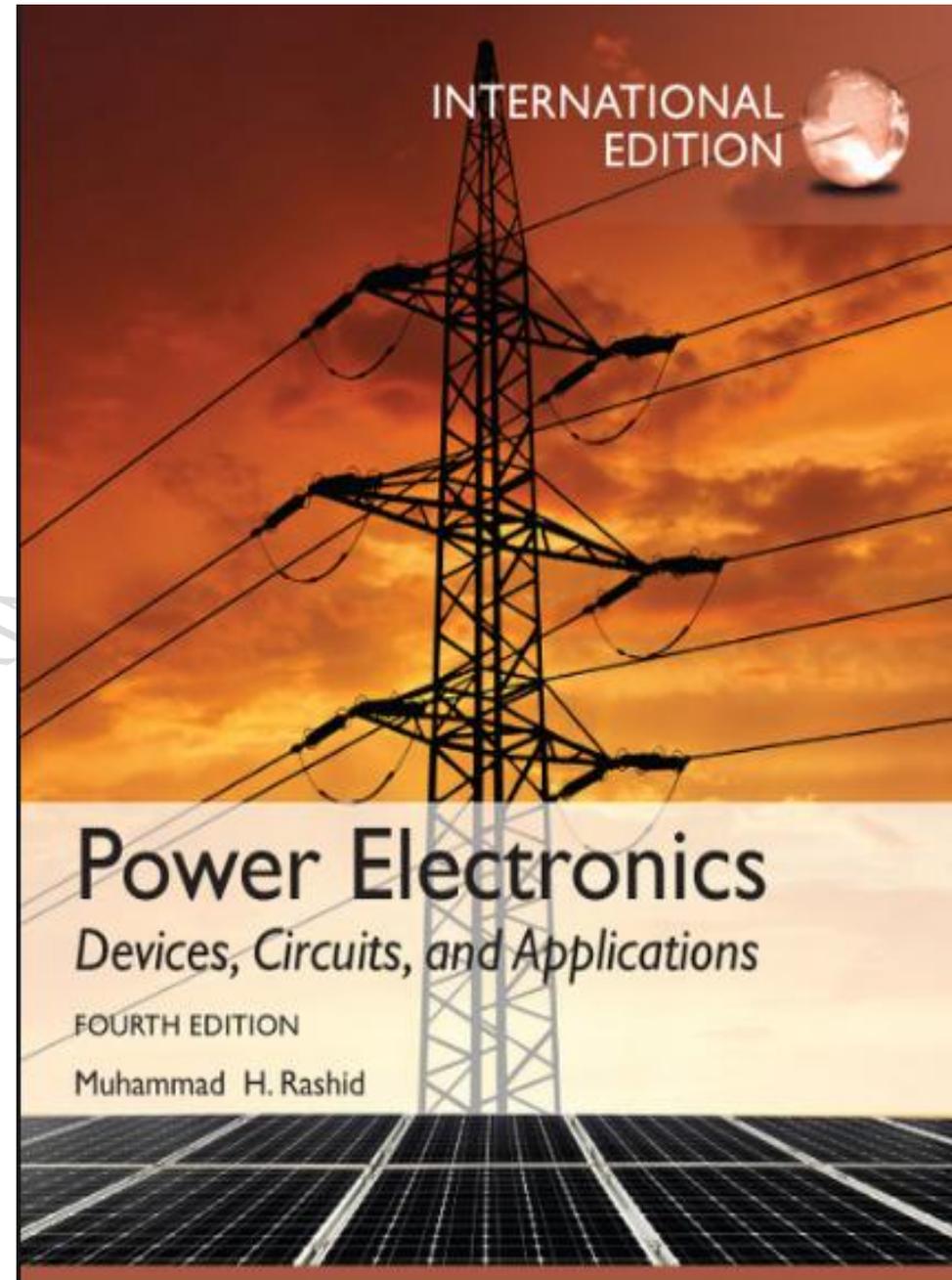A. Assuming that $n = 2$ and $V_T = 25.7$ mV, find the reverse saturation current I_S .

University of Technology
Laser and Optoelectronic Engineering
Department
Power Electronics/2018-2019)
For the third years (Laser Engineering)

Prepared by: Lec. Dr. Mothana Amaar Hassan
Laser and Optoelectronic Engineering
Department



Ref: Power Electronics 4th edition/ Muhammed H. Rashid


Lecture No.2

Reverse Recovery

- An important dynamic characteristic of a non-ideal diode is reverse recovery current
- When a diode turns off, the current in it decreases and momentarily becomes negative before becoming zero as shown in figure below.
- The diode continues to conduct due to minority carriers that remain stored in the *pn*-junction.
- The minority carriers require a certain time (t_{rr}) to recombine with opposite charges and to be neutralized.

- Effects of reverse recovery:

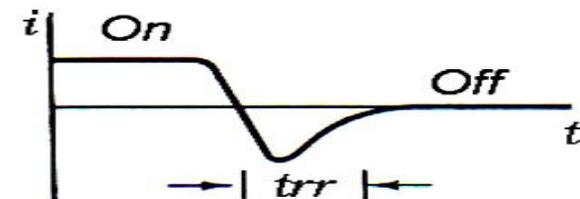
1. Switching losses increase – especially in high frequency applications,
2. Voltage rating increase,
3. Over voltage (spikes) in inductive loads.



Reverse recovery time

Reverse Recovery Characteristics

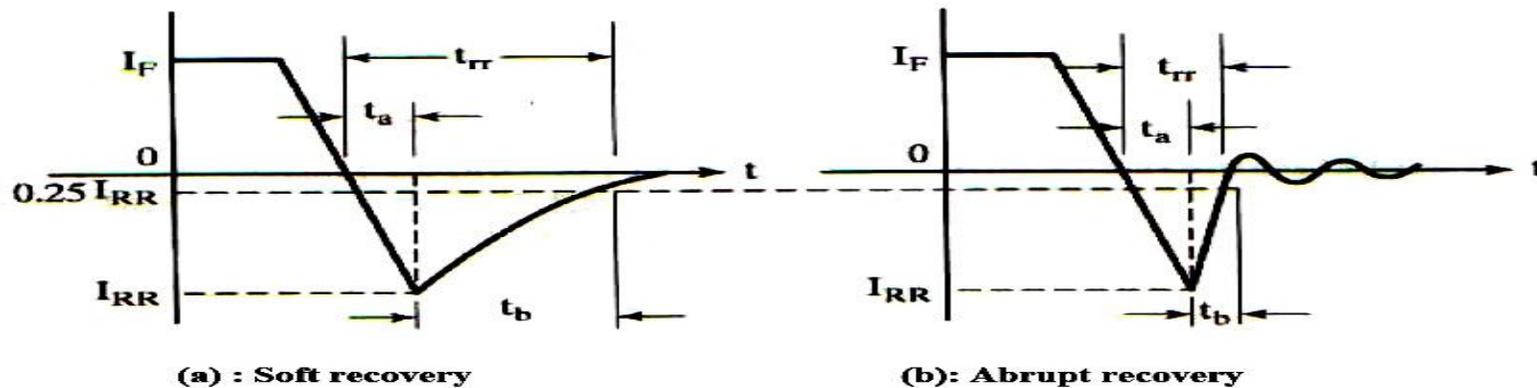- Figure shows two reverse recovery characteristics of junction diodes.



(a) : Soft recovery

(b): Abrupt recovery

- The reverse recovery time is denoted as t_{rr} and is measured from the initial zero crossing of the diode current to 25% of maximum (peak) reverse current, I_{RR} .
- t_{rr} consists of two components, t_a and t_b .
- t_a is due to charge storage in the depletion region of the junction and represents the time between the zero crossing and the peak reverse current, I_{RR} .
- t_b is due to charge stored in the bulk semiconductor material.
- The ratio t_b / t_a is known as *softness factor*, SF .
- For practical purposes, need to be concerned with the total recovery time t_{rr} and the peak value of the reverse current I_{RR} .

$$t_{rr} = t_a + t_b$$

- The peak reverse current can be expressed in reverse di/dt as:

$$I_{RR} = t_a \times \frac{di}{dt}$$

- t_{rr} is dependent on the *junction temperature*, *rate of fall of forward current*, and the *forward current* prior to commutation.
- **Reverse recovery charge, Q_{RR}** , is amount of charge carriers that flow across the diode in the reverse direction due to changeover from forward conduction to reverse blocking condition.
- **Q_{RR}** value is determined from the area enclosed by the path of the reverse recovery current.
- The storage charge, which is the area enclosed by the path of the recovery current, is approximately:

$$Q_{RR} \cong \frac{1}{2} I_{RR} t_a + \frac{1}{2} I_{RR} t_b = \frac{1}{2} I_{RR} t_{rr}$$

Or;

$$I_{RR} \cong \frac{2Q_{RR}}{t_{rr}}$$

Then;

$$t_{rr} t_a = \frac{2Q_{RR}}{di/dt}$$

If t_b is negligible as compared to t_a , which usually the case, $t_{rr} \approx t_a$, then;

$$t_{rr} \cong \sqrt{\frac{2Q_{RR}}{di/dt}}$$

And

$$I_{RR} = \sqrt{2Q_{RR} \frac{di}{dt}}$$

- The storage charge is dependent on the forward diode current, I_F .
- The **peak reverse recovery current** I_{RR} , **reverse charge** Q_{RR} , and the **softness factor** SF are very important parameters for circuit design and are normally included in the diodes specification sheets.
- A diode which is in a reverse-biased, then been forward-biased again. It also requires a certain time known as forward recovery (turn-on) time before all the majority carriers over the whole junction can contribute to the current flow.
- If the rate of rise of the forward current is high and the forward current is concentrated to a small area of the junction, the diode will fail.

Home Work:

The reverse recovery time of a diode is $t_{rr} = 3 \mu\text{s}$ and the rate of fall of the diode current is $di/dt = 30 \text{ A}/\mu\text{s}$. Determine:

- The storage charge Q_{RR}
- The peak reverse current I_{RR}

EXAMPLE (1): The manufacturer of a selected diode gives the rate of fall of the diode current $di/dt = 20 \text{ A}/\mu\text{s}$, and a reverse recovery time of $t_{rr} = 5 \mu\text{s}$. What value of peak reverse current do you expect?

SOLUTION: The peak reverse current is given as:
The storage charge Q_{RR} calculated as:

$$Q_{RR} = \frac{1}{2} \frac{di}{dt} t_{rr}^2 = 1/2 \times 20 \text{ A}/\mu\text{s} \times (5 \times 10^{-6})^2 = 50 \mu\text{C}.$$


$$I_{rr} = \sqrt{20 \frac{\text{a}}{\mu\text{s}} \times 2 \times 50 \mu\text{C}} = 44.72 \text{ A}$$

$$I_{rr} = \sqrt{\frac{di}{dt} 2Q_{RR}}$$

2. Thyristor (SCR)

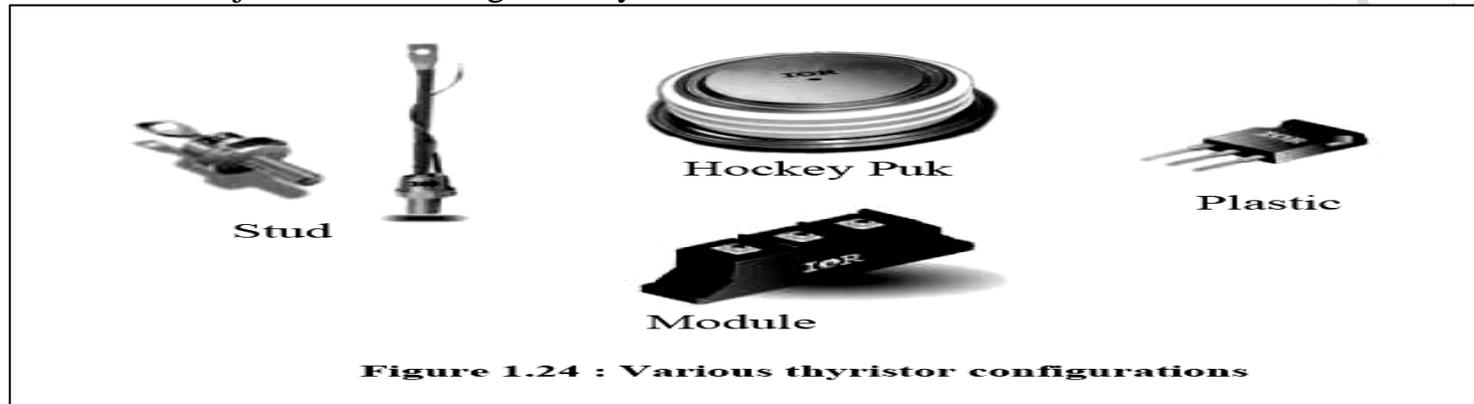
2.1 Introduction

Thyristors are usually three-terminal devices with four layers of alternating p- and n-type material (i.e. three p-n junctions) in their main power handling section. The control terminal of the thyristor, called the gate (G) electrode, may be connected to an integrated and complex structure as part of the device. The other two terminals, anode (A) and cathode (K), handle the large applied potentials and conduct the major current through the thyristor. The anode and cathode terminals are connected in series



2. Basic Structure and Operation


Figure below shows a conceptual view of a typical thyristor with the three p-n junctions and the external electrodes labeled. Also shown in the figure the thyristor circuit symbol used in electrical schematics.

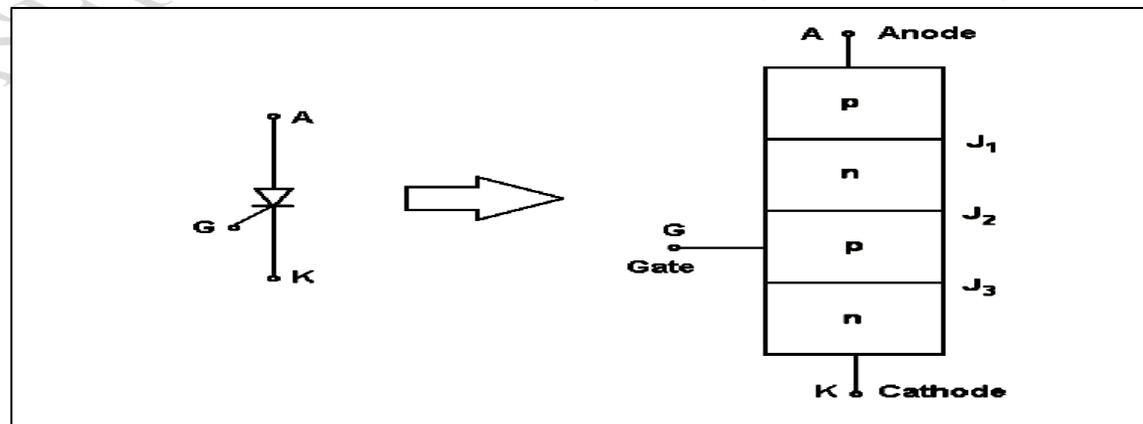

The operation of thyristors is as follows. When a positive voltage is applied to the anode (with respect to a cathode), the thyristor is in its forward-blocking state. The center junction J_2 (see Figure above) is reverse-biased. In this operating mode, the gate current is held to zero (open-circuit). In this condition only thermally generated leakage current flows through the device and can often be approximate as zero in value. When a positive gate current is injected into the device J_3 becomes forward-biased and electrons are injected from the n-emitter into the p- base. The thyristor is latched in its on state (forward-conduction).

This switching behavior can also be explained in terms of the two- transistor analog shown in Figure below. The two transistors are regenerative coupled so that if the sum of their forward current gains (α 's) exceeds unity, each drives the other into saturation. The forward current gain (expressed as the ratio of collector current to emitter current) of the pnp transistor is denoted by α_p , and that of the npn as α_n . The α 's are current dependent and increase slightly as the current increases. The center junction J_2 is reverse-biased under forward applied voltage (positive V_{AK}).


When Gate current increases the current in both transistors are increased. Collector current in the npn transistor acts as base current for the pnp, and analogously, the collector current of the pnp acts as base current driving the npn transistor. The thyristor switches to its on-state (latches). This condition can also be reached, without any gate current, by increasing the forward applied voltage so that the internal leakage current increased.

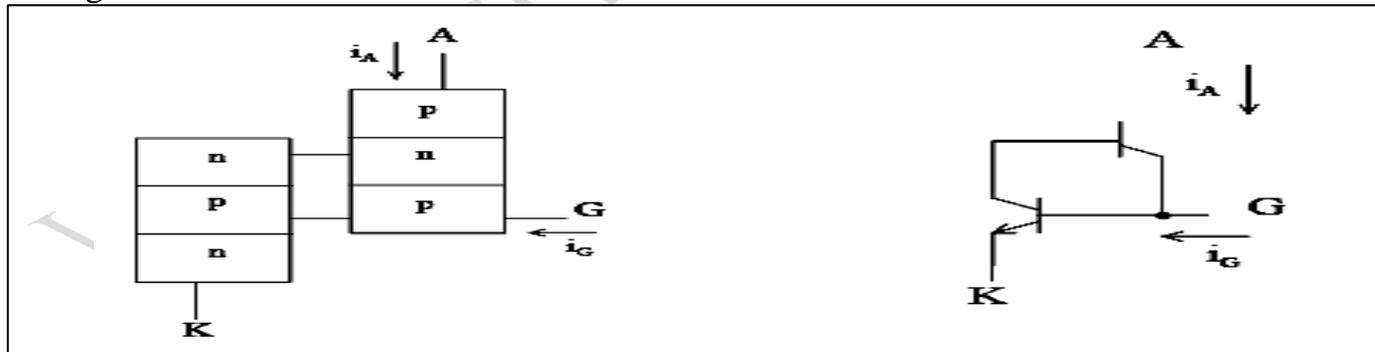

Current-Voltage Curves for Thyristors

A plot of the anode current (i_A) as a function of anode cathode voltage (V_{AK}) is shown in Figure below. The forward blocking mode is shown as the low-current portion of the graph (solid curve around operating point "1"). With zero gate current and positive V_{AK} the forward characteristic in


the "off state" or "blocking-state" is determined by the center junction J_2 , which is reverse-biased. At operating point "1", very little current flows (I_{co} only) through the device. However, if the applied voltage exceeds the forward-blocking voltage, the thyristor switches to its "on-state" or "conducting-state" (shown as operating point "2") because of carrier multiplication. The effect of gate current is to lower the blocking voltage at which switching takes place.

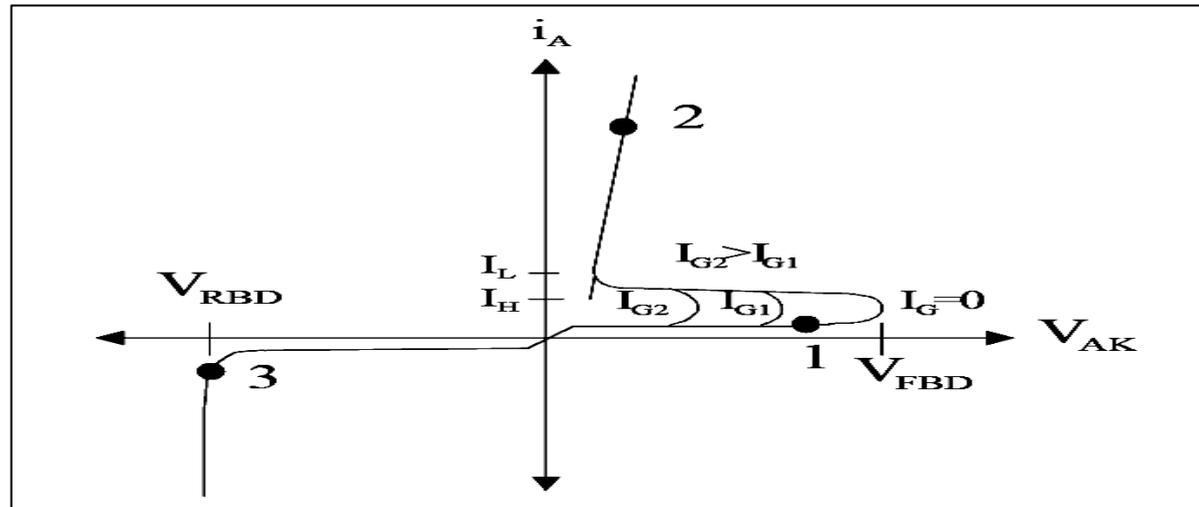

The thyristor moves rapidly along the negatively sloped portion of the curve until it reaches a stable operating point determined by the external circuit (point "2"). The portion of the graph indicating forward conduction shows the large values of i_A that may be conducted at relatively low values of V_{AK} , similar to a power diode.

University of Technology
Laser and Optoelectronic Engineering
Department
Power Electronics/2018-2019)
For the third years (Laser Engineering)

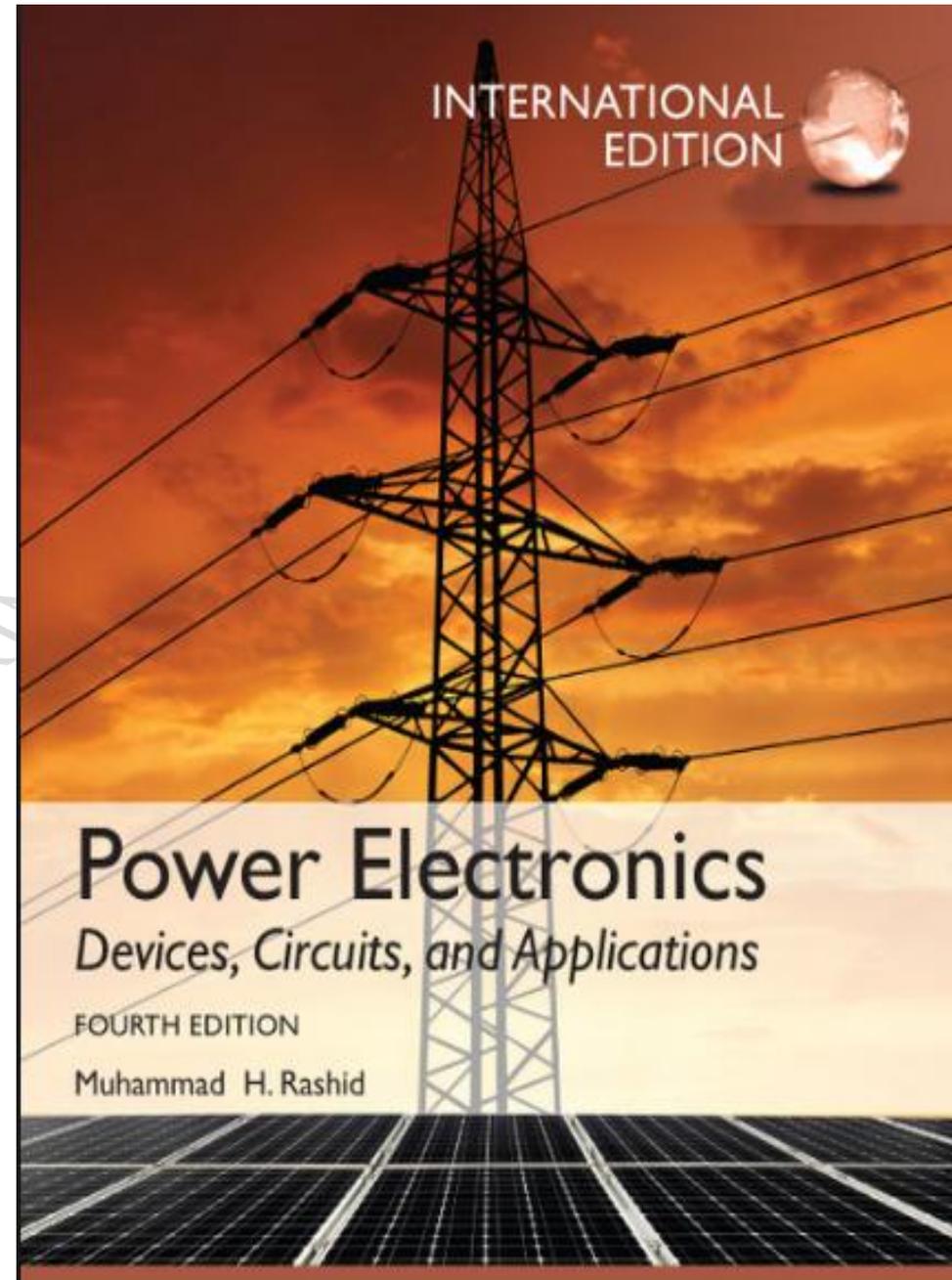Prepared by: Lec. Dr. Mothana Amaar Hassan
Laser and Optoelectronic Engineering
Department



Ref: Power Electronics 4th edition/ Muhammed H. Rashid

Lecture No.3

AC-DC converter (Rectifiers)

Introduction

Certain terms will be frequently used in this lesson and subsequent lessons while characterizing different types of rectifiers. Such commonly used terms are defined in this section.

Let “f(t)” be the instantaneous value of any voltage or current associated with a rectifier circuit, then the following terms, characterizing the properties of “f(t)”, can be defined.

Peak value of f(t) : As the name suggests f_{\max} .

Average (DC) value of f(t) is (F_{av}) : Assuming f(t) to be periodic over the time period T,
$$F_{\text{av}} = \frac{1}{T} \int_0^T f(t) dt$$

RMS (effective) value of f(t) is (F_{RMS}) : For f(t), periodic over the time period T,

$$F_{\text{RMS}} = \sqrt{\frac{1}{T} \int_0^T f^2(t) dt}$$

Form factor of f(t) is (f_{FF}) : Form factor of ‘f(t)’ is defined as:

$$f_{\text{FF}} = \frac{F_{\text{RMS}}}{F_{\text{av}}}$$

Ripple factor of f(t) is (f_{RF}) : Ripple factor of f is defined as:

$$f_{\text{RF}} = \frac{\sqrt{F_{\text{RMS}}^2 - F_{\text{av}}^2}}{F_{\text{av}}} = \sqrt{f_{\text{FF}}^2 - 1}$$

Ripple factor can be used as a measure of the deviation of the output voltage and current of a rectifier from ideal dc.

Peak to peak ripple of $f(t)$ is f_{pp} : By definition $f_{pp} = f_{\max} - f_{\min}$ Over period T

Single-Phase Diode Rectifiers

There are two types of single-phase diode rectifier that convert a single-phase ac supply into a dc voltage, namely, single-phase half-wave rectifiers and single-phase full-wave rectifiers.. For the sake of simplicity the diodes are considered to be ideal, that is, they have zero forward voltage drop and reverse recovery time. This assumption is generally valid for the case of diode rectifiers that use the mains, a low-frequency source, as the input, and when the forward voltage drop is small compared with the peak voltage of the mains.

Single-Phase Half-Wave Rectifiers(R-Load)

The simplest single-phase diode rectifier is the single-phase half-wave rectifier. A single-phase half-wave rectifier with resistive load is shown in Figure below. The circuit consists of only one diode that is usually fed with a transformer secondary as shown. During the positive half-cycle of the transformer secondary voltage, diode D conducts. During the negative half-cycle, diode D stops conducting. Assuming that the transformer has zero internal impedance and provides perfect sinusoidal voltage on its secondary winding, the voltage and current waveforms of resistive load R and the voltage waveform of diode D are shown in Figure below.

→It is clear that the peak inverse voltage (PIV) of diode D is equal to V_m .

→Hence the Peak Repetitive Reverse Voltage (V_{RRM}) rating of diode D must be chosen to be higher than V_m to avoid reverse breakdown.

→ The Peak Repetitive Forward Current (I_{FRM}) rating of diode D must be chosen to be higher than the peak load current V_m/R .


The average value of the load voltage v_L is V_{dc} and it is defined as:
$$V_{dc} = \frac{1}{T} \int_0^T v_L(t) dt$$

That load voltage $V_L(t)=0$, for the negative half-cycle. Note that the angular frequency of the source $\omega=2\pi/T$. Then:

$$V_{dc} = \frac{1}{2\pi} \int_0^{\pi} V_m \sin \omega t d(\omega t)$$

Therefore,

$$V_{dc} = \frac{V_m}{\pi} = 0.318 V_m$$

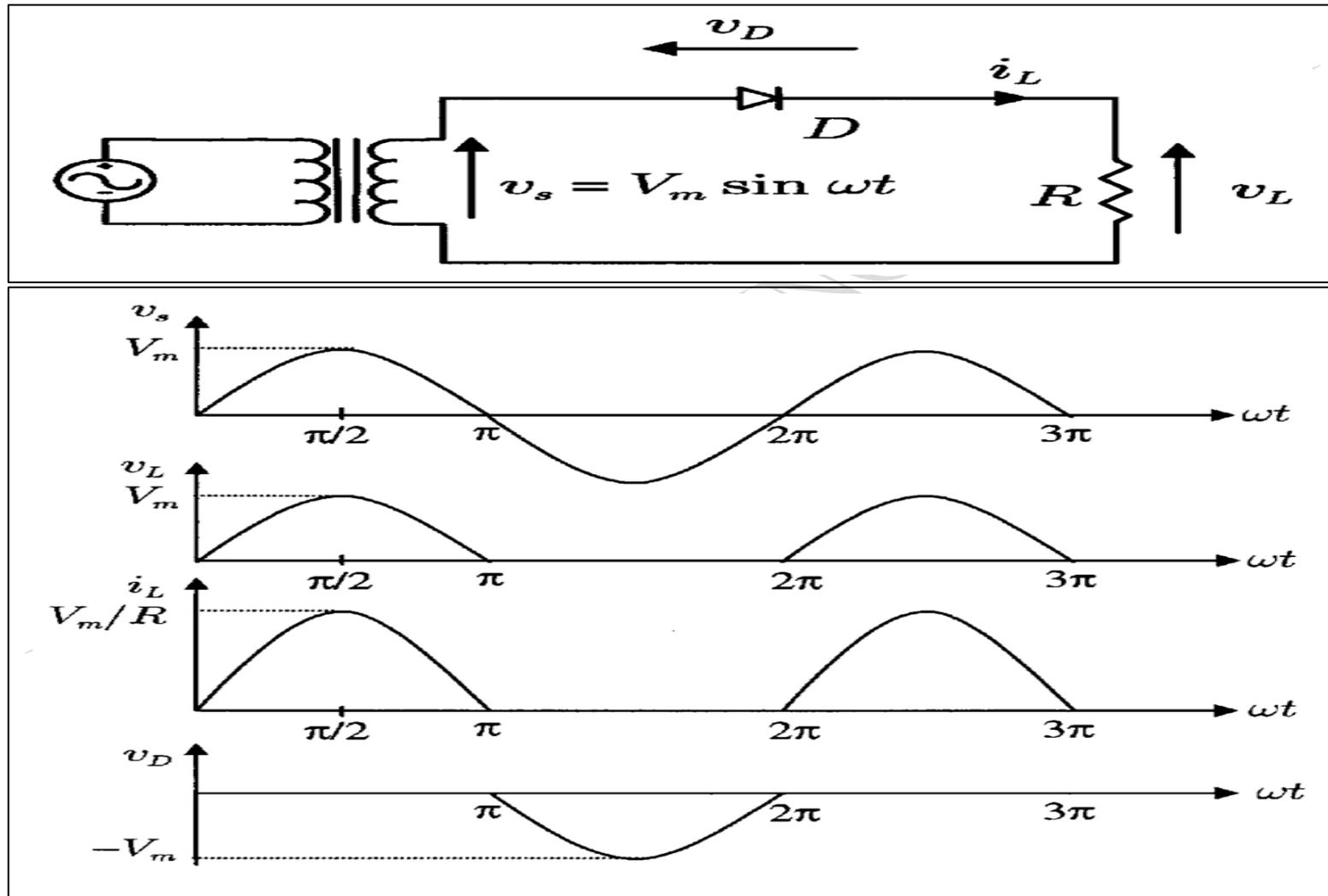

The root-mean-square (rms) value of load voltage v_L is V_L , which is defined as:

$$V_L = \left[\frac{1}{T} \int_0^T v_L^2(t) dt \right]^{1/2}$$

In the case of a half-wave rectifier, $V_L(t)=0$ for the negative half-cycle, therefore,

$$V_L = \sqrt{\frac{1}{2\pi} \int_0^\pi (V_m \sin \omega t)^2 d(\omega t)}$$

Or;

$$V_L = \frac{V_m}{2} = 0.5 V_m$$

The average value of load current i_L is I_{dc} and because load R is purely resistive it can be found as:

$$I_{dc} = \frac{V_{dc}}{R}$$

The root-mean-square (rms) value of load current i_L is I_L and it can be found as:

$$I_L = \frac{V_L}{R}$$

In the case of a half-wave rectifier, And

$$I_{dc} = \frac{0.318 V_m}{R}$$

→ The rectification ratio, which is a figure of merit for comparing the effectiveness of rectification, is defined as:

$$\frac{P_{dc}}{P_L} = \frac{V_{dc} I_{dc}}{V_L I_L}$$

In the case of a half-wave diode rectifier, the rectification ratio can be determined by:

$$= \frac{(0.318 V_m)^2}{(0.5 V_m)^2} = 40.5\%$$

→ The form factor (FF) is defined as the ratio of the root-mean square value of a voltage or current to its average value,

$$\mathbf{FF} = \frac{V_L}{V_{dc}} \quad \text{or} \quad \frac{I_L}{I_{dc}}$$

$$\mathbf{FF} = \frac{0.5 V_m}{0.318 V_m} = 1.57$$

→The ripple factor (RF), which is a measure of the ripple content, is defined as:

$$\mathbf{RF} = \frac{V_{ac}}{V_{dc}}$$

Where V_{ac} is the effective (rms) value of the ac component of load voltage V_L ,


$$V_{ac} = \sqrt{V_L^2 - V_{dc}^2}$$

$$\mathbf{RF} = \sqrt{\left(\frac{V_L}{V_{dc}}\right)^2 - 1} = \sqrt{\mathbf{FF}^2 - 1}$$

$$\mathbf{RF} = \sqrt{1.57^2 - 1} = 1.21$$

University of Technology
Laser and Optoelectronic Engineering
Department
Power Electronics/2018-2019)
For the third years (Laser Engineering)

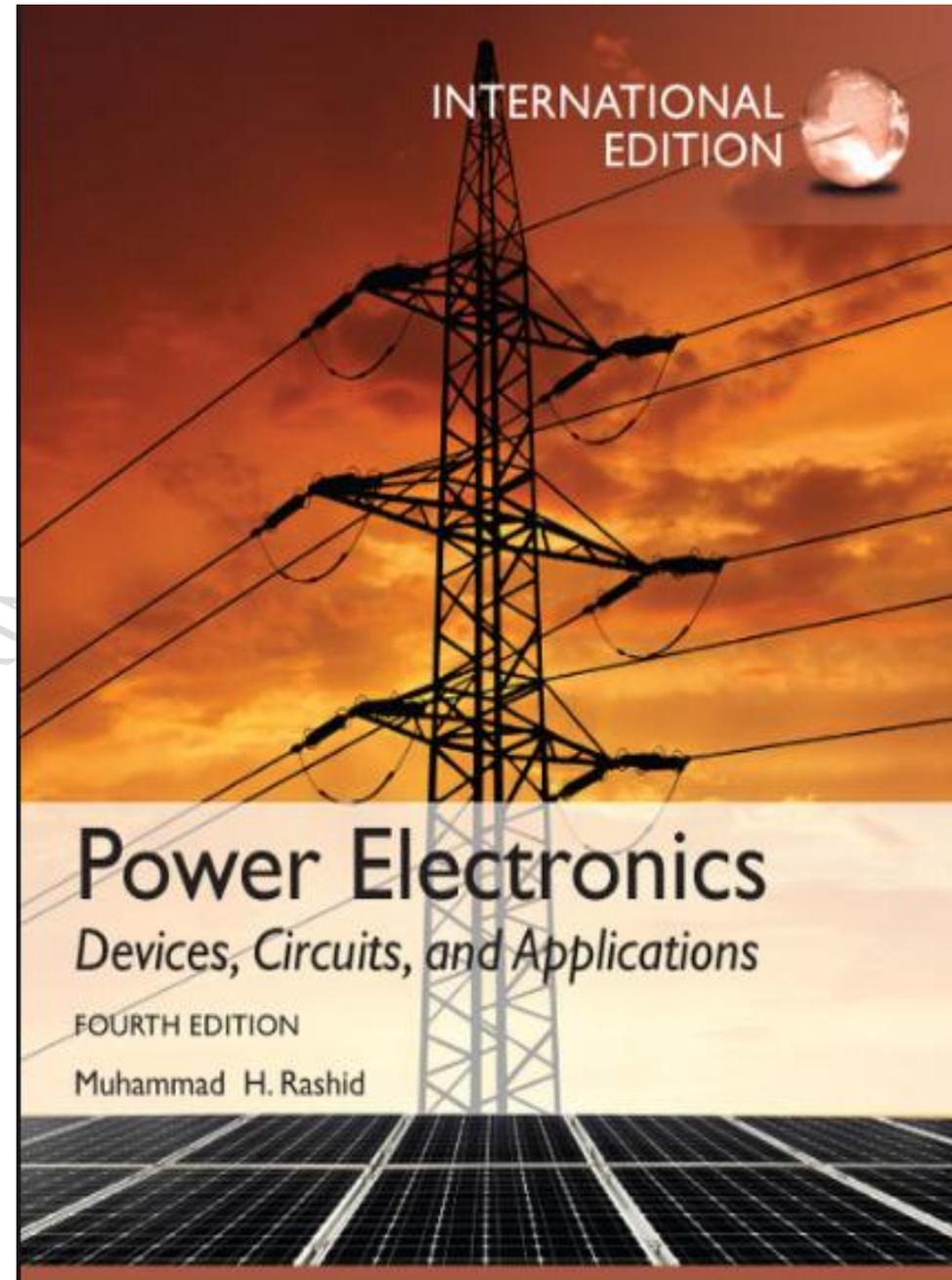Prepared by: Lec. Dr. Mothana Amaar Hassan
Laser and Optoelectronic Engineering
Department





Ref: Power Electronics 4th edition/ Muhammed H. Rashid

Lecture No.4

Single Phase Half-Wave Rectifier (RL- Load)

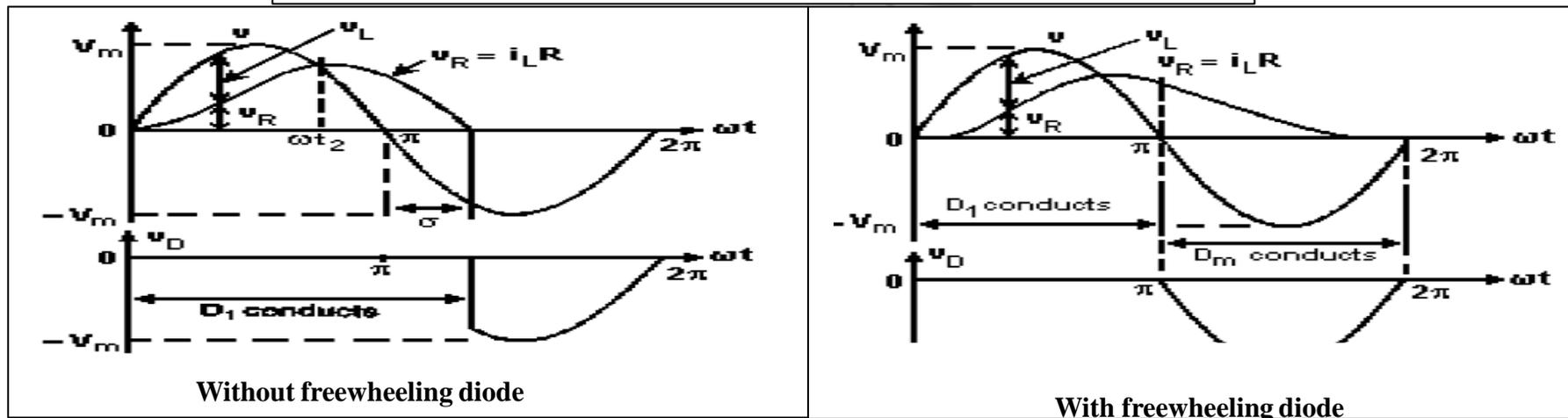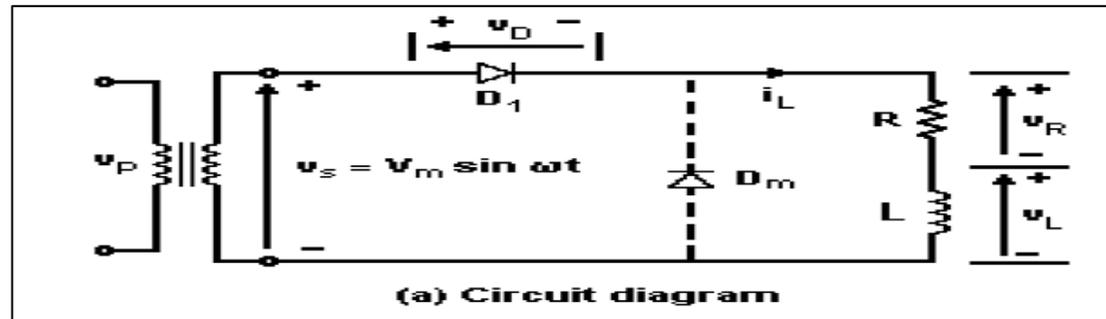The half wave rectifier with an inductive load (RL) is shown in figure below.



During the interval 0 to $\pi/2$

The source voltage V_s increases from zero to its positive maximum, while the voltage across the inductor V_L opposes the change of current through the load. It must be noted that the current through an inductor cannot change instantaneously; hence, the current gradually increases until it reaches its maximum value. The current does not reach its peak when the voltage is at its maximum, which is consistent with the fact that the current through an inductor lags the voltage across it. During this

time, energy is transferred from the ac source and is stored in the magnetic field of the inductor.

For the interval $\pi/2$ and π

The source voltage decreases from its positive maximum to zero. The induced voltage in the inductor reverses polarity and opposes the associated decrease in current, thereby aiding the diode forward current. Therefore, the current starts decreasing gradually at a delayed time, becoming zero when all the energy stored by then inductor is released to the circuit. Again, this is consistent with the fact that current lags voltage in an inductive circuit. Hence, even after the source voltage has dropped past zero volts, there is still load current, which exists a little more than half a cycle.

For the interval greater than π

At π , the source voltage reverses and starts to increase to its negative maximum. However, the voltage induced across the inductor is still positive and will sustain forward conduction of the diode until this induced voltage decreases to zero. When this induced voltage falls to zero, the diode will now be reversed biased, but would have conducted forward current for an angle β , where $\beta = \pi + \sigma$. σ is the extended angle of current conduction due to the energy stored in the magnetic field being returned to the source.

The instantaneous supply voltage V_s is given by:

$$V_s = V_R + V_L$$

For angles, less than ωt_2 the inductor is storing energy in its magnetic field from the source and the inductor voltage would be such as to oppose the growth of current and the supply voltage. For angles greater than ωt_2 the inductor voltage would have reversed and would aid the supply voltage to prevent the fall of current. Hence, the average inductor voltage is zero.

From the preceding discussion

-For $0 \leq \omega t \leq \beta$

$$v_o = v_i \quad i_o = i_i$$

For $\beta \leq \omega t \leq 2\pi$

$$v_o = 0$$

$$i_o = i_i = 0$$

$$v_D = v_i - v_o = v_i$$

The average output voltage is given by:

$$\begin{aligned} V_{dc} &= \frac{1}{2\pi} \int_0^{2\pi} v_o d\omega t = \frac{1}{2\pi} \int_0^{\beta} \sqrt{2} V_i \sin \omega t d\omega t \\ &= \frac{\sqrt{2} V_i}{\pi} \left(\frac{1 - \cos \beta}{2} \right) \end{aligned}$$

Where, $V_m = \sqrt{2} V_i$

The rms output voltage is given by:

$$\begin{aligned} V_L &= \sqrt{\frac{1}{2\pi} \int_0^{\beta} 2 V_i^2 \sin^2 \omega t d\omega t} \\ &= \sqrt{\frac{V_i^2}{2\pi} \left(\beta - \frac{1}{2} \sin 2\beta \right)} = \frac{V_i}{\sqrt{2}} \sqrt{\frac{2\beta - \sin 2\beta}{2\pi}} \end{aligned}$$

$$FF = \frac{V_L}{V_{dc}} = \pi \sqrt{\frac{2\beta - \sin 2\beta}{2\pi(1 - \cos \beta)^2}}$$

$$\begin{aligned} RF &= \sqrt{FF^2 - 1} \\ &= \sqrt{\frac{\pi(2\beta - \sin 2\beta)}{2(1 - \cos \beta)^2} - 1} \end{aligned}$$

All these quantities are functions of β which can be found as follows.

-For $0 \leq \omega t \leq \beta$

$$\begin{aligned} v_i &= \sqrt{2} V_i \sin \omega t = L \frac{di_o}{dt} + R i_o \\ i_o (\omega t = 0) &= i_o (\omega t = \beta) = 0 \end{aligned}$$

The solution is given by:

$$i_o = I_0 e^{-\frac{\omega t}{\tan\phi}} + \frac{\sqrt{2}V_i}{Z} \sin(\omega t - \phi)$$

Where;

$$\tan\phi = \frac{\omega L}{R} \quad Z = \sqrt{R^2 + \omega^2 L^2}$$

The addition of a freewheeling diode

The average dc voltage varies proportionately to $[1 - \cos(\beta)]$. This can be made to be a maximum, thereby increasing the average dc voltage, by making $\cos(\beta)$ a minimum. The maximum value that this can take is given by $\cos(\pi + \sigma) = -1$, which can be obtained if $\sigma = \pi$. We can make $\sigma = \pi$ with the addition of a freewheeling diode given by D_m as shown with the dotted line.

When the supply voltage goes to zero, the current from D_1 is transferred across to diode D_m . This is called commutation of diodes. The result is the charge in the inductor will be used to keep diode D_m on, instead of

previously forcing D_1 to remain in its forward state. This would reduce the value of the extended angle of conduction of the diode D_1 , σ to zero.

We can see that if the value of the inductance is high, it will store more charge and therefore be able to keep diode D_m on for a longer time.


Then the inductor would be able to keep diode D_m on for the entire duration of the negative half cycle, and by so doing, maintain a continuous load current.

Home work: Consider the circuit shown with:

- i) Purely resistive load.
- ii) Resistive-inductive load.

Then determine the following factors:

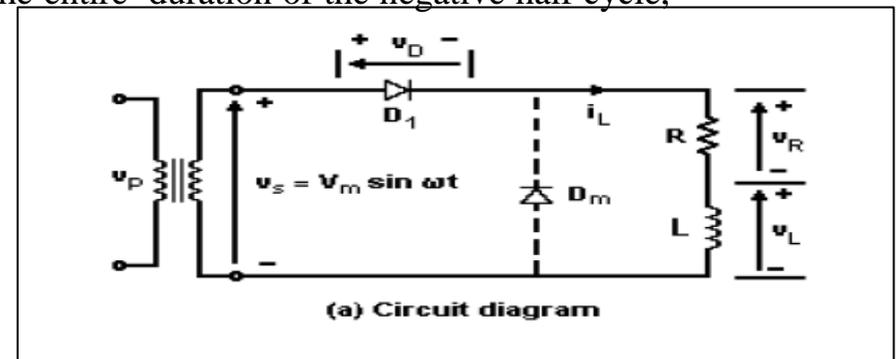
- a. The efficiency
- b. The ripple factor
- c. The peak inverse voltage (PIV) of diode D_1
- d. Form factor



$$R=110\Omega, L=100\text{mH}, V_s=30\text{V}$$

University of Technology
Laser and Optoelectronic Engineering
Department
Power Electronics/2018-2019)
For the third years (Laser Engineering)

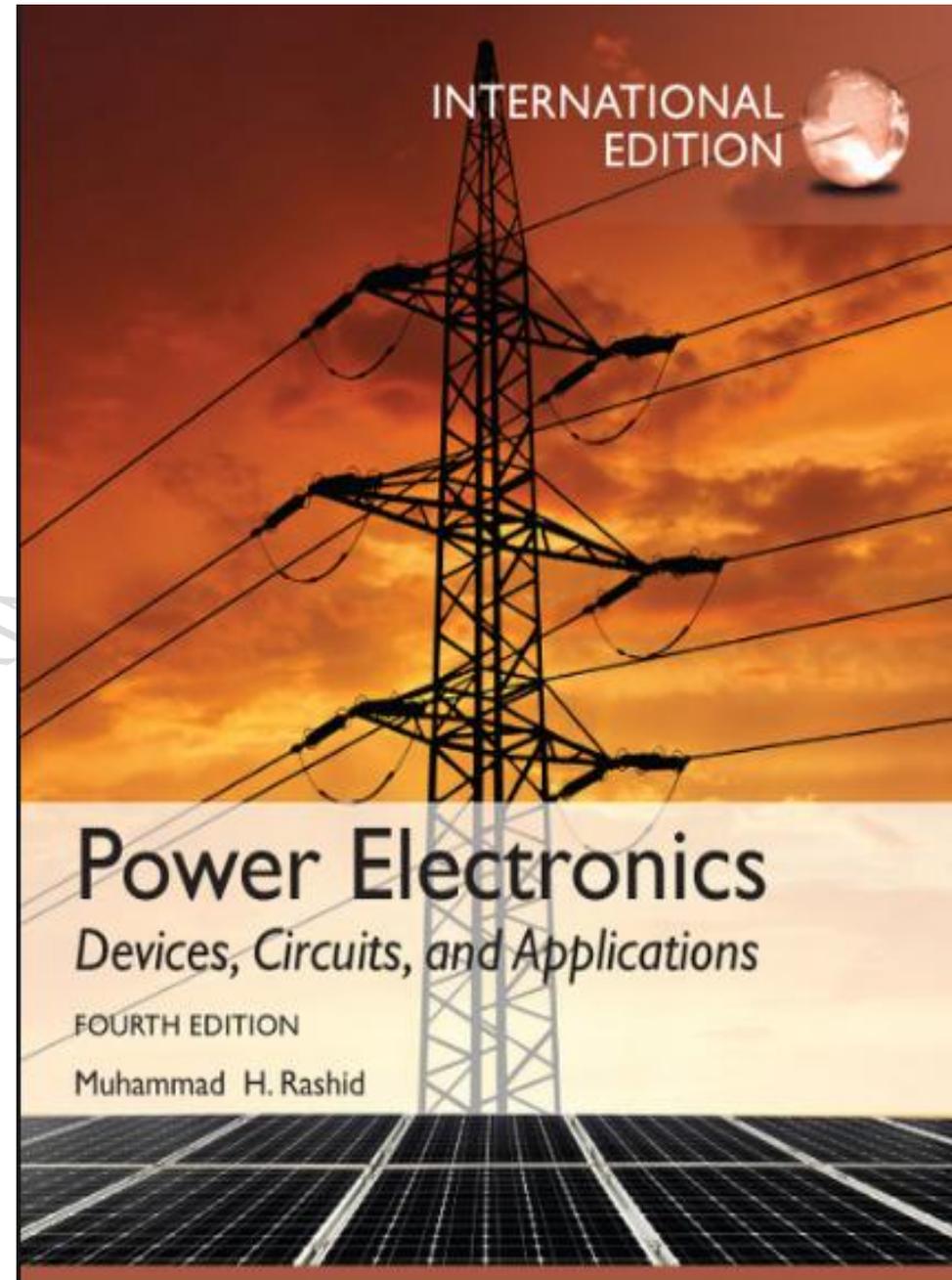Prepared by: Lec. Dr. Mothana Amaar Hassan
Laser and Optoelectronic Engineering
Department




Ref: Power Electronics 4th edition/ Muhammed H. Rashid


Lecture No.5

High Voltage Series Connected Diodes

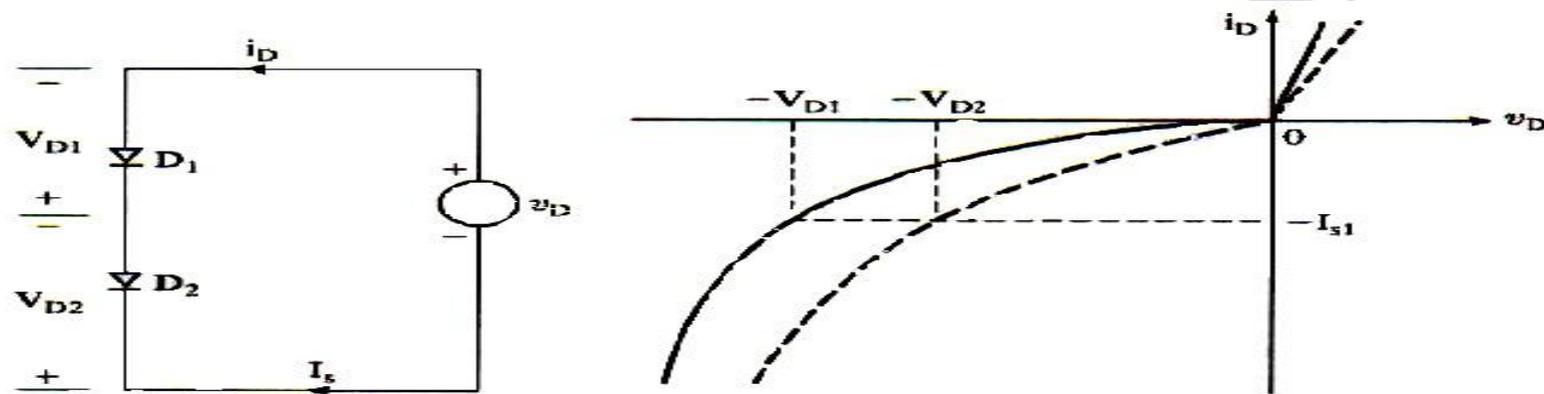- In many high voltage applications, one commercially diode cannot meet the required voltage rating
- Because of this reason, diodes are connected in series to increase the reverse blocking capabilities.



- V_{D1} and V_{D2} are the sharing reverse voltages of diodes D_1 and D_2 .
- In practice, the $v-i$ characteristics for the same type of diodes differ due to tolerances in their production process.
- Refer to the figure above, for reverse blocking conditions, each diode has to carry the same leakage current. And as a result, the blocking voltage will be different.
- The solution is to force equal voltage sharing by connecting a resistor across each diode as shown in figure below.
- This will make the leakage current of each diode would be different because the total leakage current must be shared by a diode and its resistor.

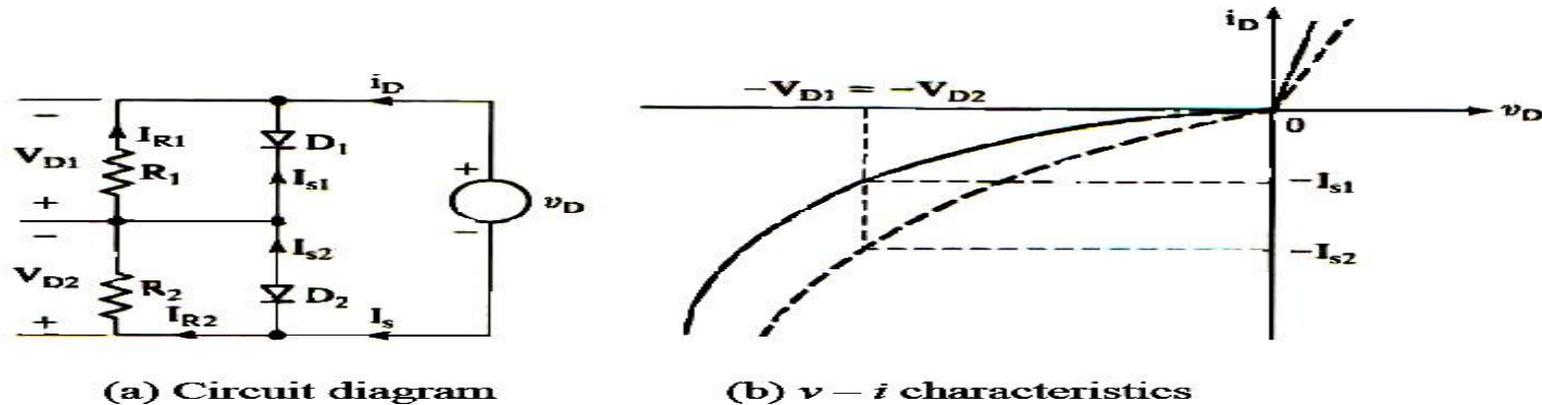

$$V_{D1} + V_{D2} = V_S$$

$$I_S = I_{S1} + I_{R1} = I_{S2} + I_{R2}$$

$$I_{R1} = \frac{V_{D1}}{R_1} \quad \text{and} \quad I_{R2} = \frac{V_{D2}}{R_2}$$

$$I_{S1} + \frac{V_{D1}}{R_1} = I_{S2} + \frac{V_{D2}}{R_2}$$

Howe work:

Two diodes are connected in series, shown in figure above to share a total dc reverse voltage of $V_D = 5\text{kV}$. The reverse leakage currents of the two diodes are $I_{S1}=30\text{mA}$ and $I_{S2}=35\text{mA}$.

a) Find the diode voltages if the voltage sharing resistance are equal,

$$R_1=R_2=R=100\text{k}\Omega.$$

b) Find the voltage sharing resistances R_1 and R_2 if the diode voltages are equal, $V_{D1}=V_{D2}=0.5V_D$

Voltage Multiplier


Voltage multipliers may also be used as primary power supplies where a 177 volt-ac input is rectified to pulsating dc. This dc output voltage may be increased (through use of a voltage multiplier) to as much as 1000 volts dc. This voltage is generally used as the plate or screen grid voltage for electron tubes.

Voltage multipliers may be classified as voltage doublers, triplers, or quadruplers. The classification depends on the ratio of the output voltage to the input voltage. For example, a voltage multiplier that increases the


peak input voltage twice is called a voltage doubler. Voltage multipliers increase voltages through the use of series-aiding voltage sources.

Half wave voltage multiplier

Figure below shows the schematic for a half-wave voltage doubler. Notice the similarities between this schematic and those of half-wave voltage rectifiers. In fact, the doubler shown is made up of two half-wave voltage rectifiers. C_1 and D_1 make up one half-wave rectifier, and C_2 and D_2 make up the other. The schematic of the first half-wave rectifier is indicated by the dark lines in figure below. The dotted lines and associated components represent the other half-wave rectifier and load resistor.

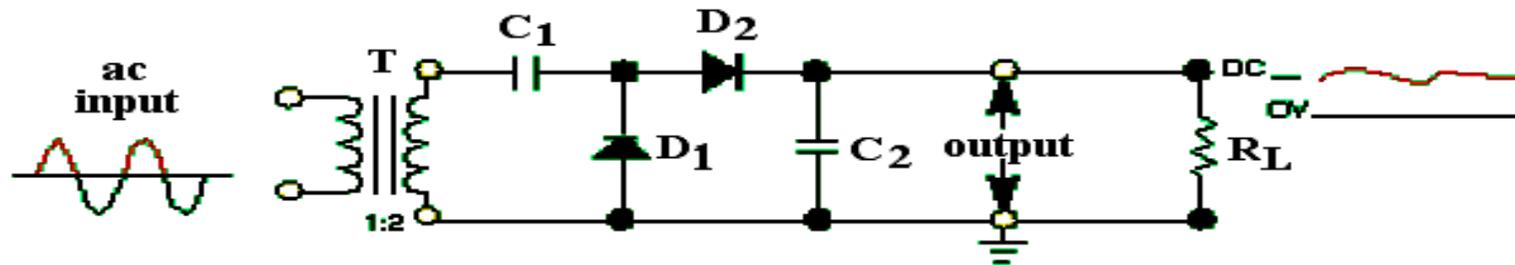


Notice that C_1 and D_1 work exactly like a half-wave rectifier. During the positive alternation of the input cycle, the polarity across the secondary winding of the transformer is make the top of the secondary is negative. At this time D_1 is forward biased (cathode negative in respect to the anode). This forward bias causes D_1 to function like a closed switch and allows current to follow the path indicated by the arrows. At this time, C_1 charges to the peak value of the input voltage.

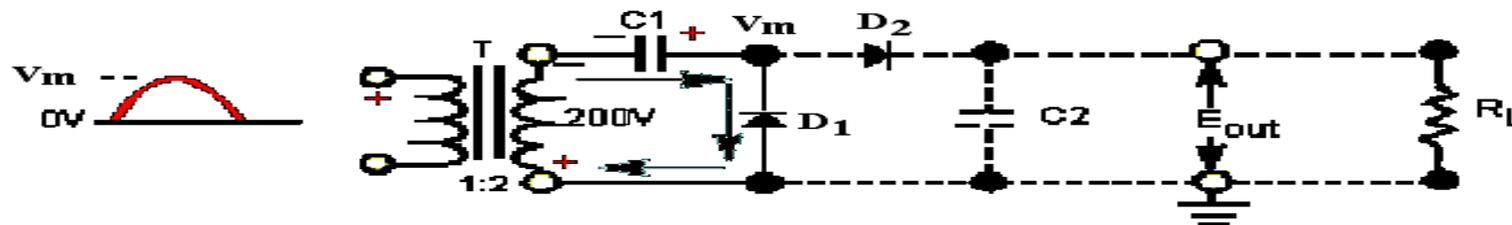

During the period when the input cycle is negative, the polarity across the secondary of the transformer is reversed. Note specifically that the top of the secondary winding is now positive. This condition now forward biases D_2 and reverse biases D_1 . A series circuit now exists consisting of

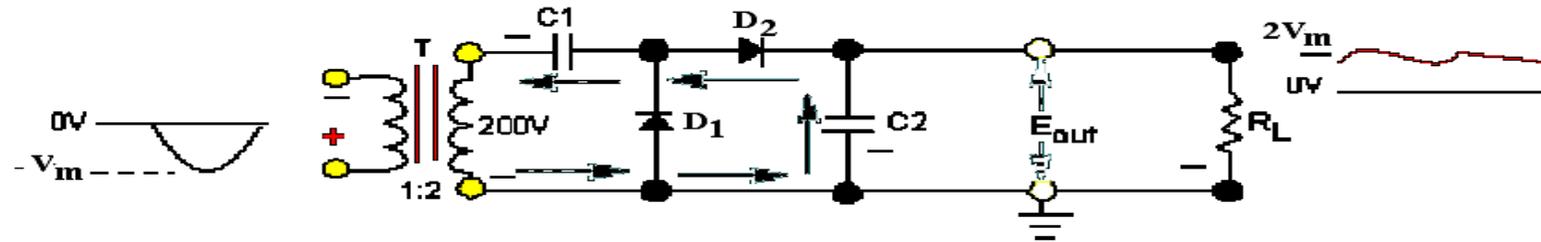
C_1 , D_2 , C_2 , and the secondary of the transformer. The secondary voltage of the transformer now aids the voltage on C_1 . This results in a pulsating dc voltage with $2V_m$, as shown by the waveform. The effect of series aiding is comparable to the connection of two batteries in series. As shown in figure C_2 charges to the sum of these voltages.



LASER ENGINEERING BRA

University of Technology
Laser and Optoelectronic Engineering
Department
Power Electronics/2018-2019)
For the third years (Laser Engineering)

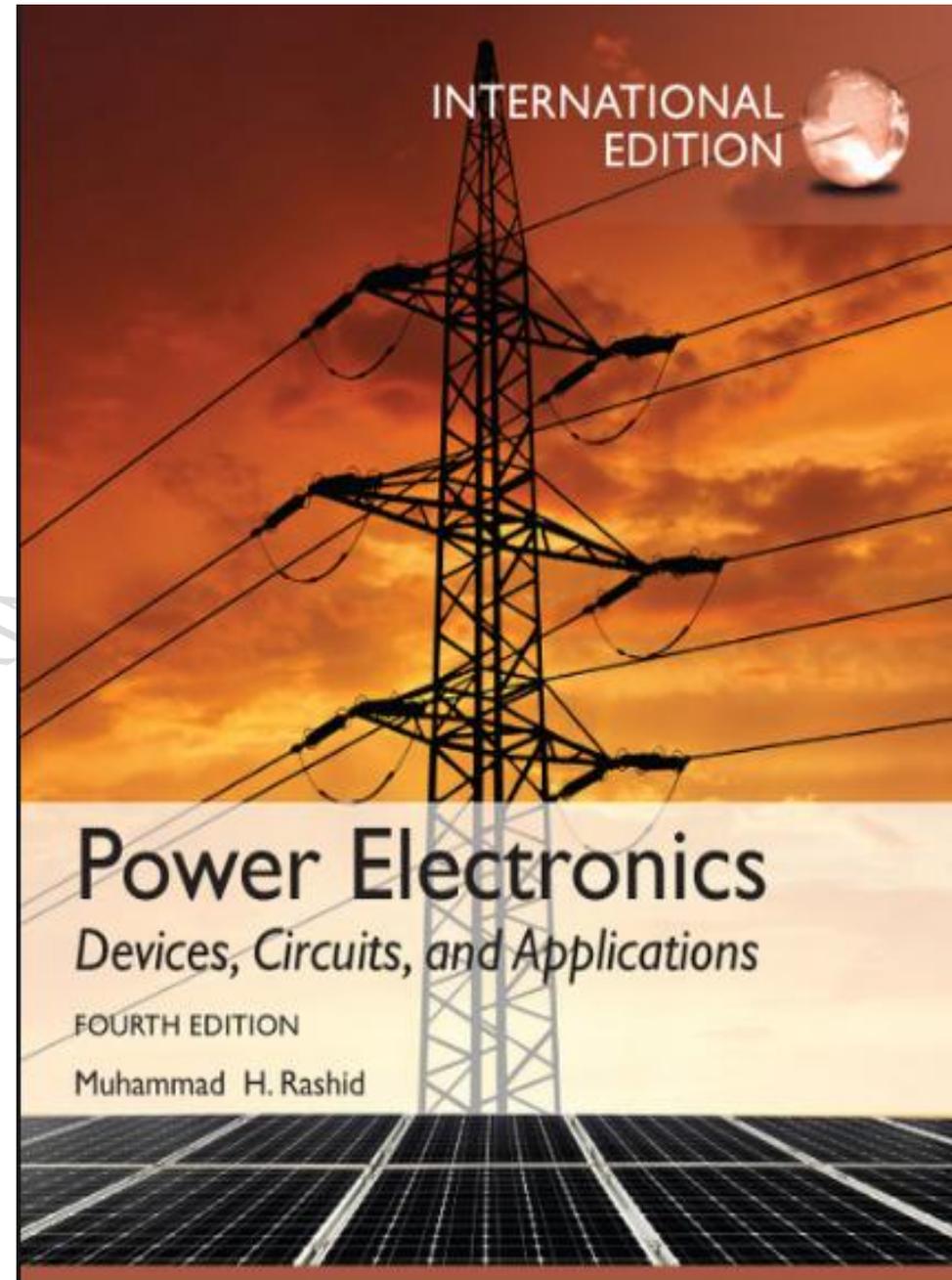Prepared by: Lec. Dr. Mothana Amaar Hassan
Laser and Optoelectronic Engineering
Department




Ref: Power Electronics 4th edition/ Muhammed H. Rashid


Lecture No. 6

Cascade Voltage Multiplier

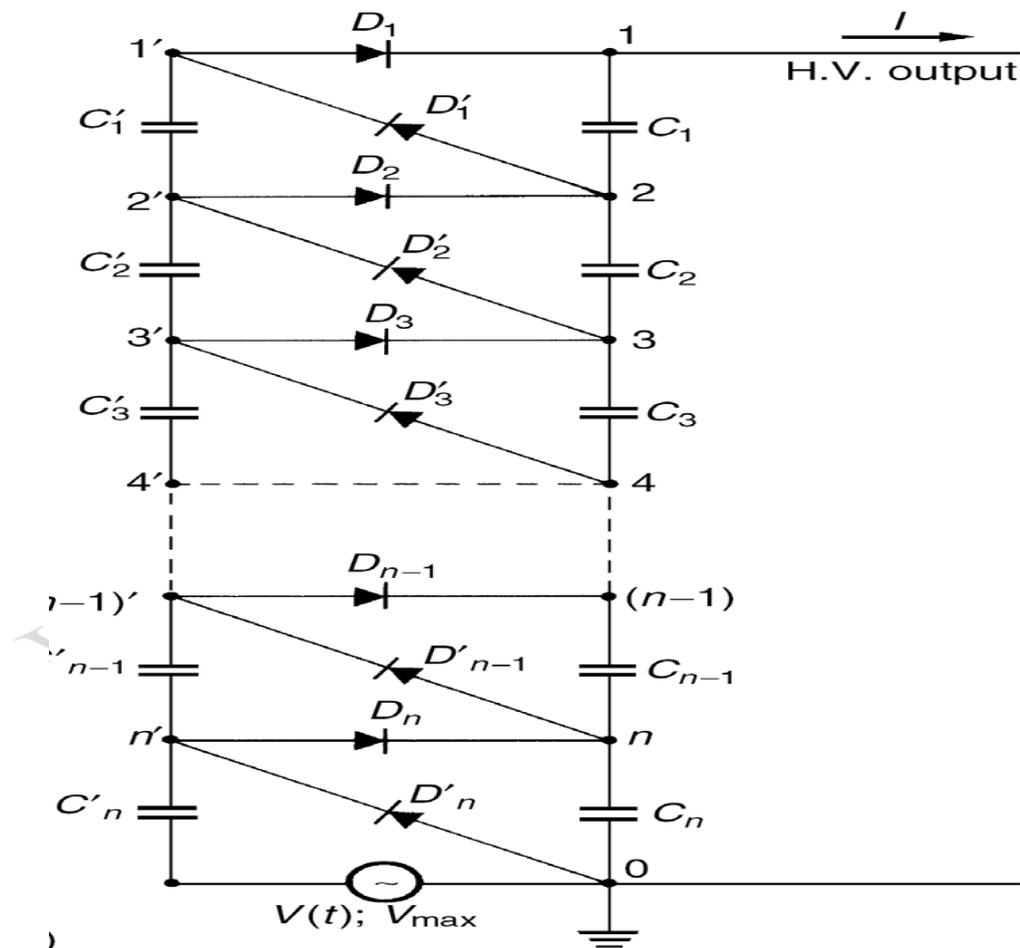To demonstrate the principle only, an n-stage single-phase cascade circuit of the 'Cockcroft-Walton type', shown in figure below, will be presented.



HV output open-circuited: $I = 0$. The portion (0 - n' - V(t)) is a half-wave rectifier circuit in which C'_n charges up to a voltage of $+V_{max}$ if $V(t)$ has reached the lowest potential, $-V_{max}$. If C'_n is still uncharged, the rectifier D_n conducts as soon as $V(t)$ increases. As the potential of point n' swings up to $+V_{2max}$ during the period $T = 1/f$, point n attains further on a steady potential of $+2V_{max}$ if $V(t)$ has reached the highest potential of $+V_{max}$. The part (n' - n - 0) is therefore a half-wave rectifier, in which the voltage across D'_n can be assumed to be the a.c. voltage source.

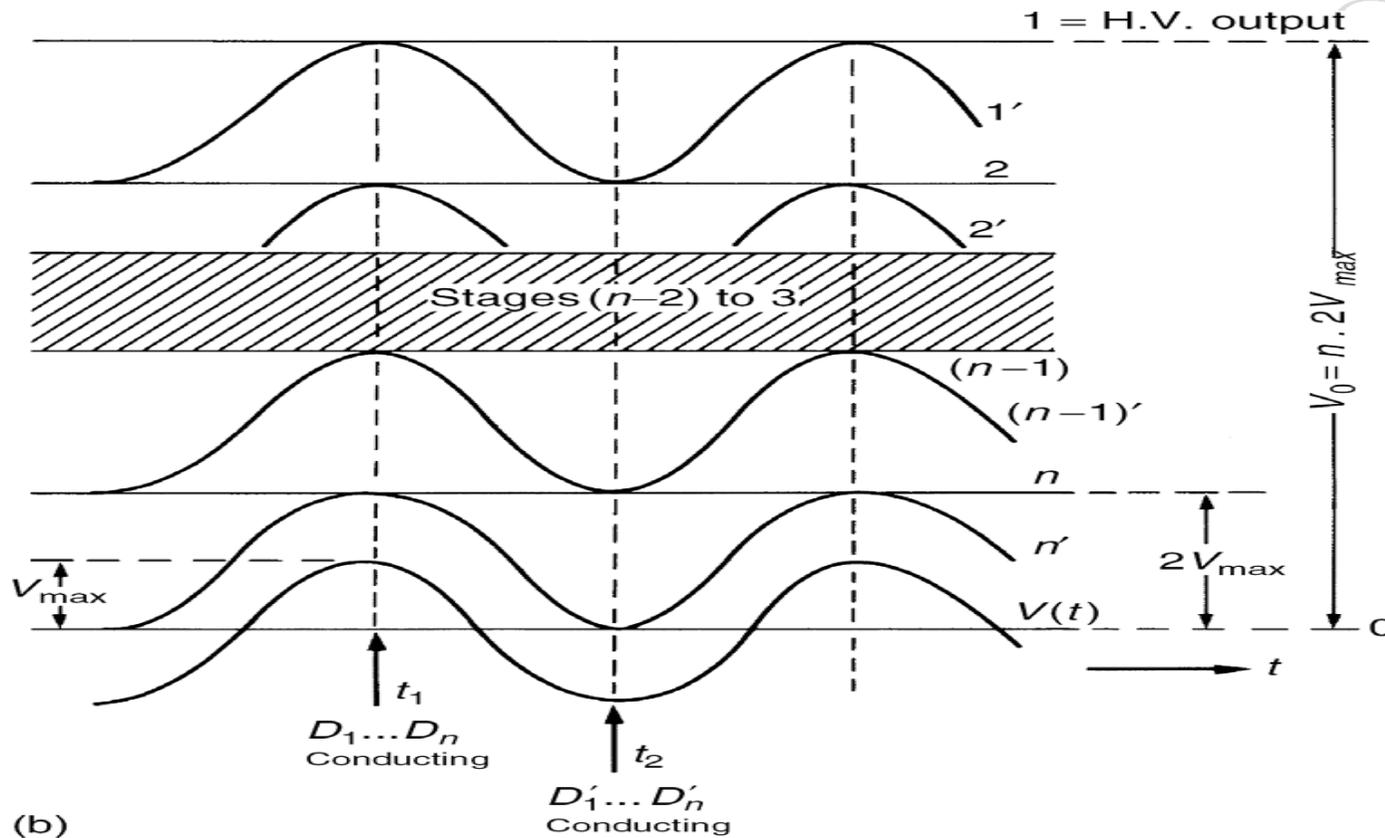


The current through D_n that charged the capacitor C_n was not provided by D'_n , but from $V(t)$ and C'_n . We can assume that the voltage across C_n is not reduced if the potential n' oscillates between zero and $+2V_{max}$. If the potential of n' , however, is zero, the capacitor C'_{n-1} is also charged to the

potential of n , i.e. to a voltage of $+2V_{\max}$. The next voltage oscillation of $V(t)$ from $-V_{\max}$ to $+V_{\max}$ will force the diode D_{n-1} to conduct, so that also C_{n-1} will be charged to a voltage of $+2V_{\max}$.

The steady state potentials at all nodes of the circuit are sketched for the circuit for zero load conditions. From this it can be seen, that:

- 1 The potentials at the nodes ($1', 2' \dots n'$) are oscillating due to the voltage oscillation of $V(t)$;
- 2 The potentials at the nodes ($1, 2 \dots n$) remain constant with reference to ground potential;
- 3 The voltages across all capacitors are of d.c. type, the magnitude of which is $2V_{\max}$ across each capacitor stage, except the capacitor C_n which is stressed with V_{\max} only;
- 4 Every rectifier $D_1, D'_1 \dots D_n, D'_n$ is stressed with $2V_{\max}$ or twice a.c. peak voltage; and
- 5 The HV output will reach a maximum voltage of $2nV_{\max}$.

H.V. output loaded: $I > 0$. If the generator supplies any load current I , the output voltage will never reach the value $2nV_{\max}$. There will also be a ripple on the voltage, and therefore we have to deal with two quantities: the voltage drop ΔV_o and the peak-to-peak ripple $2\delta V$. The sketch in figure below shows the shape of the output voltage and the definitions of ΔV_o and $2\delta V$.

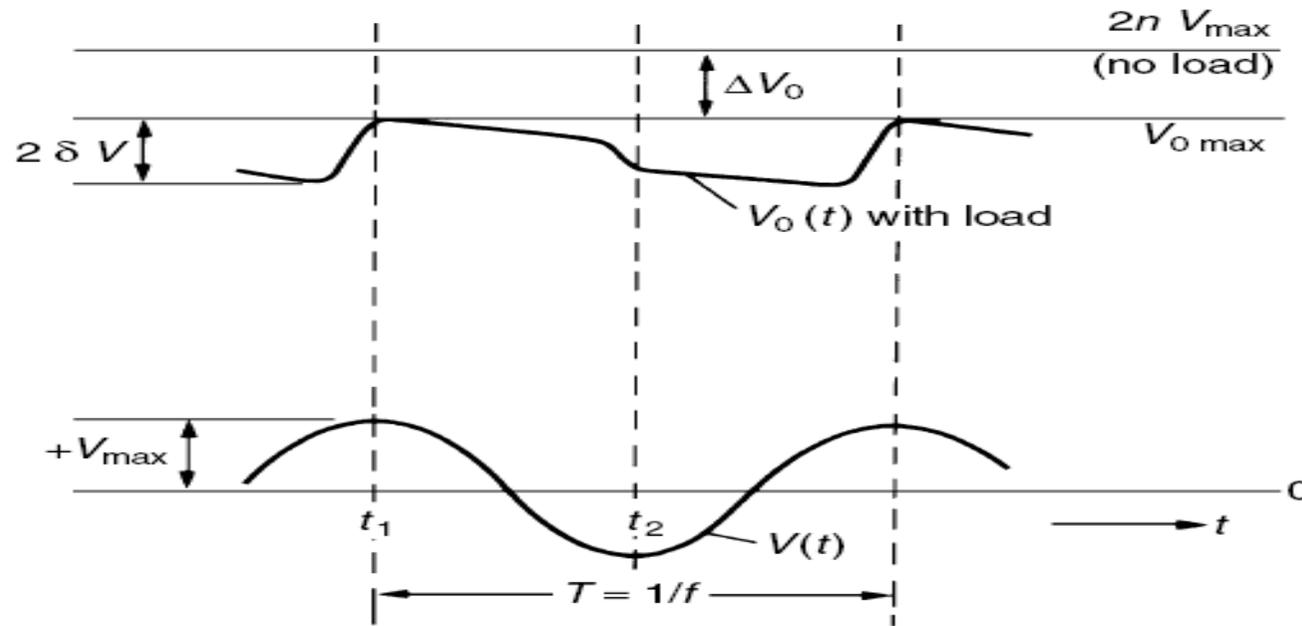

Let a charge q be transferred to the load per cycle, which is obviously $q = I \times T$. This charge comes from the smoothing column, the series connection of $C_1 \dots C_n$. If no charge would be transferred during T from this stack via $D'_1 \dots D'_n$ to the oscillating column. However, just before the time instant t_2 every diode $D'_1 \dots D'_n$ transfers the same charge q , and each of these charges discharges all capacitors on the smoothing column between the relevant node and ground potential, the ripple will be:

$$\delta v = \frac{I}{2f} \left(\frac{1}{C_1} + \frac{2}{C_2} + \frac{3}{C_3} + \dots + \frac{n}{C_n} \right)$$

Thus in a cascade multiplier the lowest capacitors are responsible for most ripple and it would be desirable to increase the capacitance in the lower stages. This is, however, very inconvenient for H.V. cascades, as a voltage breakdown at the load would completely overstress the smaller capacitors within the column. Therefore, equal capacitance values are usually provided, and with $C = C_1 = C_2 = C_3 \dots C_n$,

$$\delta V = \frac{I}{fC} \times \frac{n(n+1)}{4}$$

To calculate the total voltage drop ΔV_o , we will first consider the stage n . Although the capacitor C'_n at time t_1 will be charged up to the full voltage V_{\max} , if ideal rectifiers and no voltage drop within the a.c.-source are assumed,

$$\Delta V_o = \frac{I}{fC} \left(\frac{2n^3}{3} + \frac{n^2}{2} - \frac{n}{6} \right)$$


For a given number of stages, this maximum voltage or also the mean value $V_o = V_{o\max} - \delta V$ will decrease linearly with the load current I at constant

Where $V_{o\max} = 2nV_{\max} - \Delta V_o$

LASER ENGINEERING BRANCH

University of Technology
Laser and Optoelectronic Engineering
Department
Power Electronics/2018-2019)
For the third years (Laser Engineering)

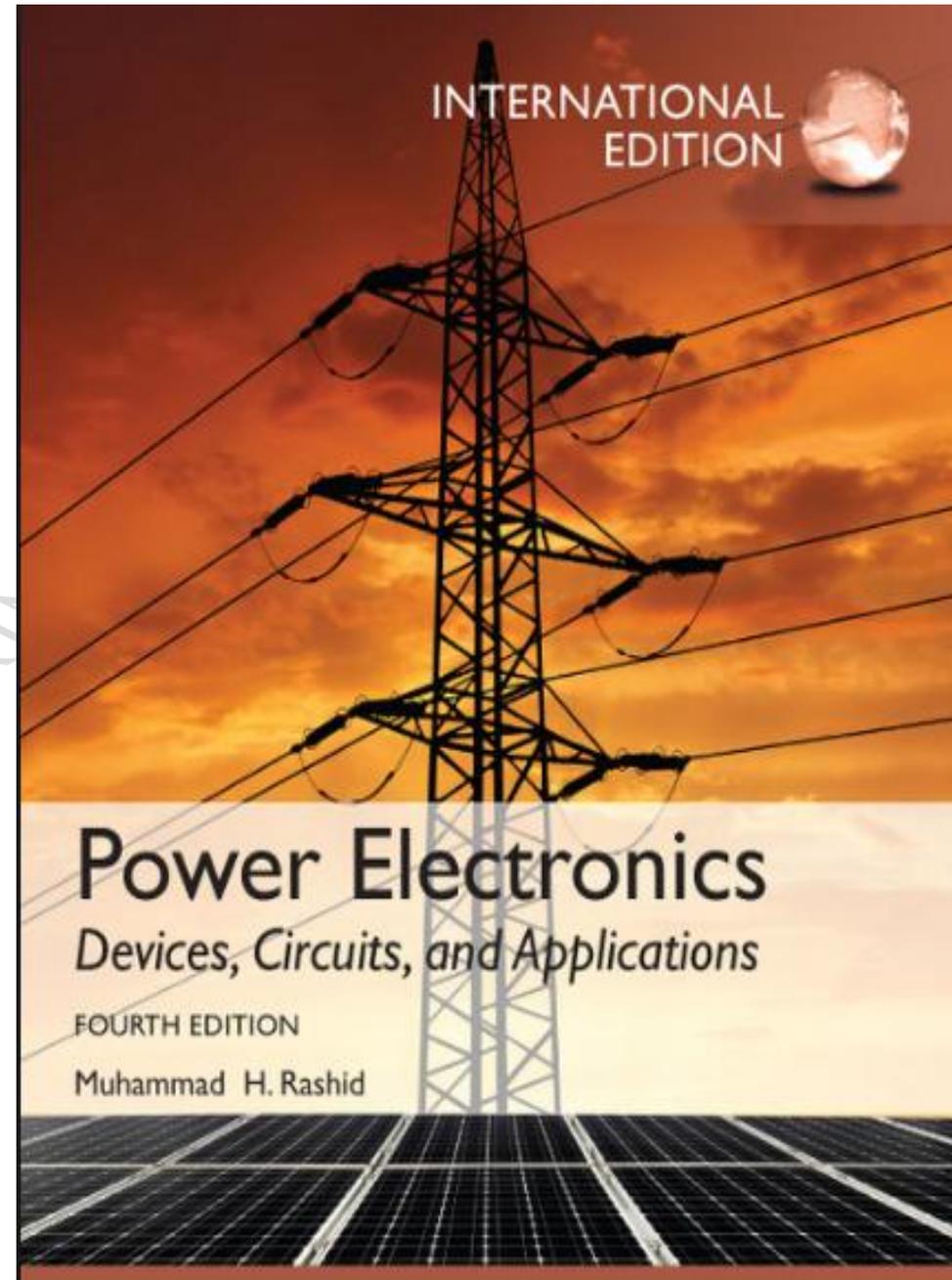Prepared by: Lec. Dr. Mothana Amaar Hassan
Laser and Optoelectronic Engineering
Department



Ref: Power Electronics 4th edition/ Muhammed H. Rashid



Lecture No.7

Single-Phase Full-Wave Rectifiers

There are two types of single-phase full-wave rectifier, namely, full-wave rectifiers with center-tapped transformer and bridge rectifiers.

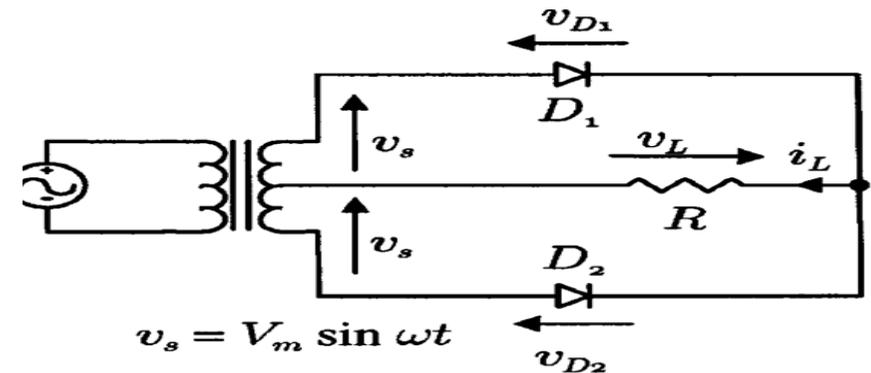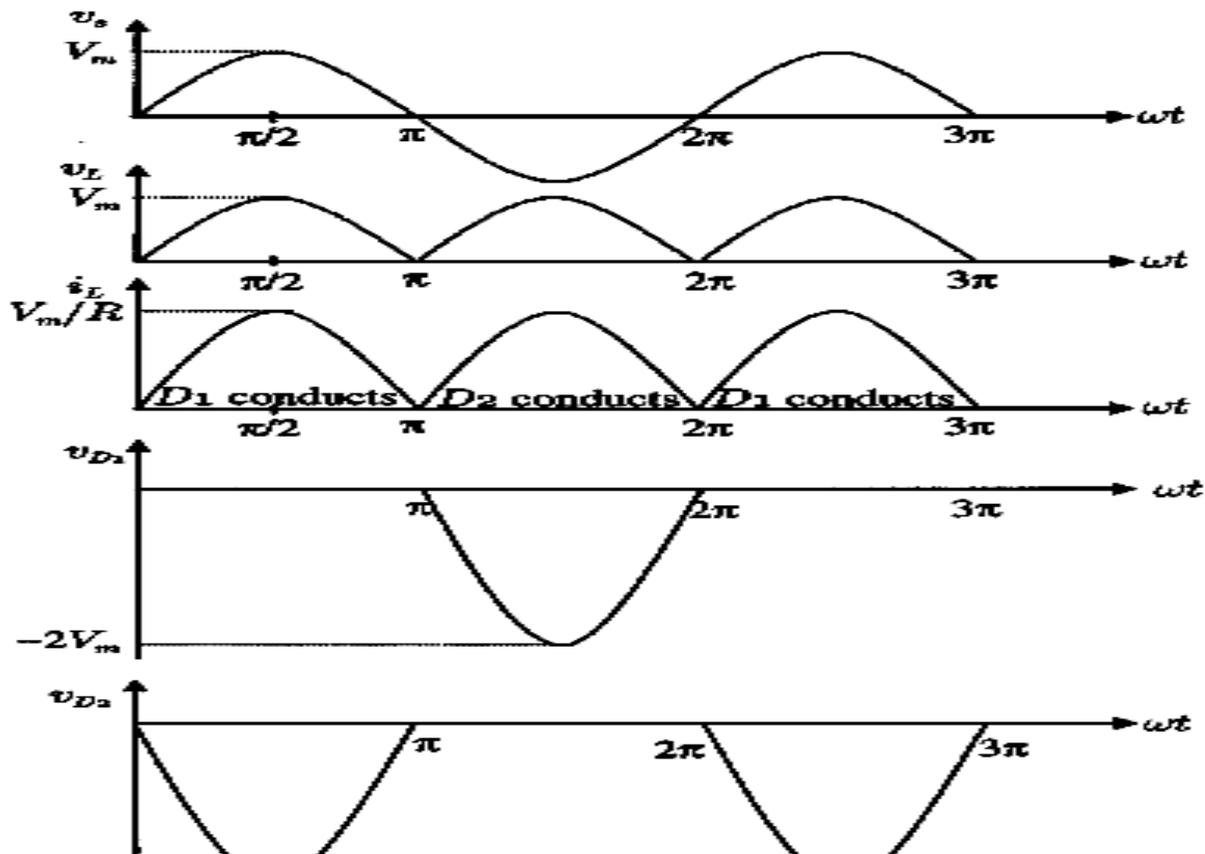I. full-wave rectifier with a center-tapped transformer:

It is clear that each diode, together with the associated half of the transformer, acts as a half-wave rectifier. The outputs of the two half-wave rectifiers are combining to produce full-wave rectification in the load.





→It is clear that the peak inverse voltage (PIV) of the diodes is equal to $2V_m$ during their blocking state.

Hence, the Peak Repetitive Reverse Voltage (V_{RRM}) rating of the diodes must be chosen to be higher than $2V_m$ to avoid reverse breakdown.

→During its conducting state, each diode has a forward current that is

equal to the load current and, therefore, the Peak Repetitive Forward Current (I_{FRM}) rating of these diodes must be chosen to be higher than the peak load current V_m/R in practice.

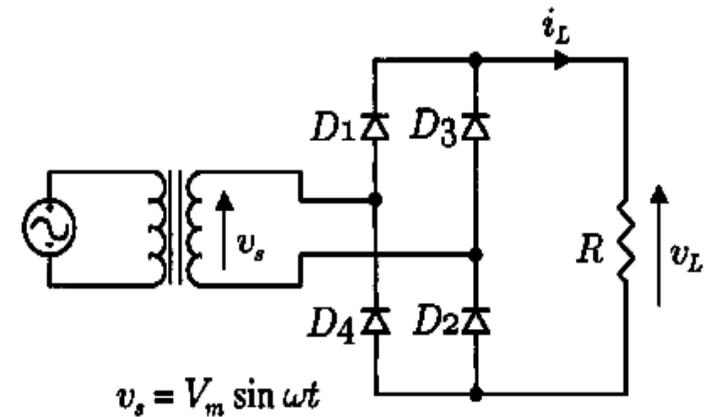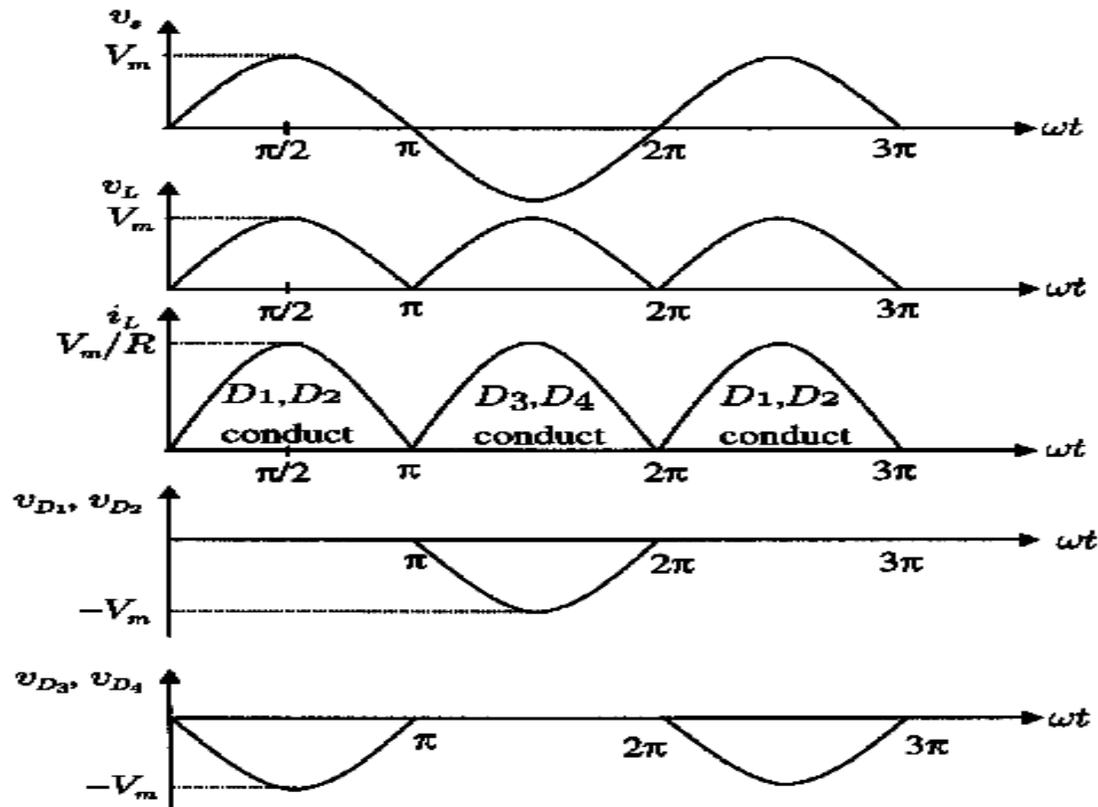Bridge rectifier: It can provide full-wave rectification without using a center-tapped transformer. During the positive half cycle of the transformer secondary voltage, the current flows to the load through diodes D_1 and D_2 . During the negative half cycle, D_3 and D_4 conduct.



→As with the full-wave rectifier with center-tapped transformer, the Peak Repetitive Forward Current (I_{FRM}) rating of the employed diodes must be chosen to be higher than the peak load current $V_m = I_m \times R$

→ However, the peak inverse voltage (PIV) of the diodes is reduced from $2V_m$ to V_m during their blocking state.

$$V_{dc} = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t d(\omega t) = V_m |\sin \omega t| \text{ for both the positive and negative half-cycles. Hence;}$$

Therefore;

$$\text{Full-wave } V_{dc} = \frac{2V_m}{\pi} = 0.636 V_m$$

The root-mean-square (rms) value of load voltage v_L is V_L , which is defined as:

$$V_L = \left[\frac{1}{T} \int_0^T v_L^2(t) dt \right]^{1/2}$$

Hence, the equation can be rewritten as:

$$V_L = \sqrt{\frac{1}{\pi} \int_0^{\pi} (V_m \sin \omega t)^2 d(\omega t)}$$

OR

$$\text{Full-wave } V_L = \frac{V_m}{\sqrt{2}} = 0.707 V_m$$

Therefore; the average and the rms value load current is:

$$I_{dc} = \frac{0.636 V_m}{R}$$

$$I_L = \frac{0.707 V_m}{R}$$

The rectification ratio is:

$$\frac{P_{dc}}{P_L} = \frac{V_{dc} I_{dc}}{V_L I_L}$$

$$= \frac{(0.636 V_m)^2}{(0.707 V_m)^2} = 81\%$$

The FF can be found by:

$$\mathbf{FF} = \frac{V_L}{V_{dc}} \quad \text{or} \quad \frac{I_L}{I_{dc}}$$

$$\mathbf{FF} = \frac{0.707 V_m}{0.636 V_m} = 1.11$$

The ripple factor (RF), which is a measure of the ripple content, is defined as:

$$\mathbf{RF} = \frac{V_{ac}}{V_{dc}}$$


$$V_{ac} = \sqrt{V_L^2 - V_{dc}^2}$$

$$\mathbf{RF} = \sqrt{\left(\frac{V_L}{V_{dc}}\right)^2 - 1} = \sqrt{\mathbf{FF}^2 - 1}$$

$$\mathbf{RF} = \sqrt{1.11^2 - 1} = 0.482$$

University of Technology
Laser and Optoelectronic Engineering
Department
Power Electronics/2018-2019)
For the third years (Laser Engineering)

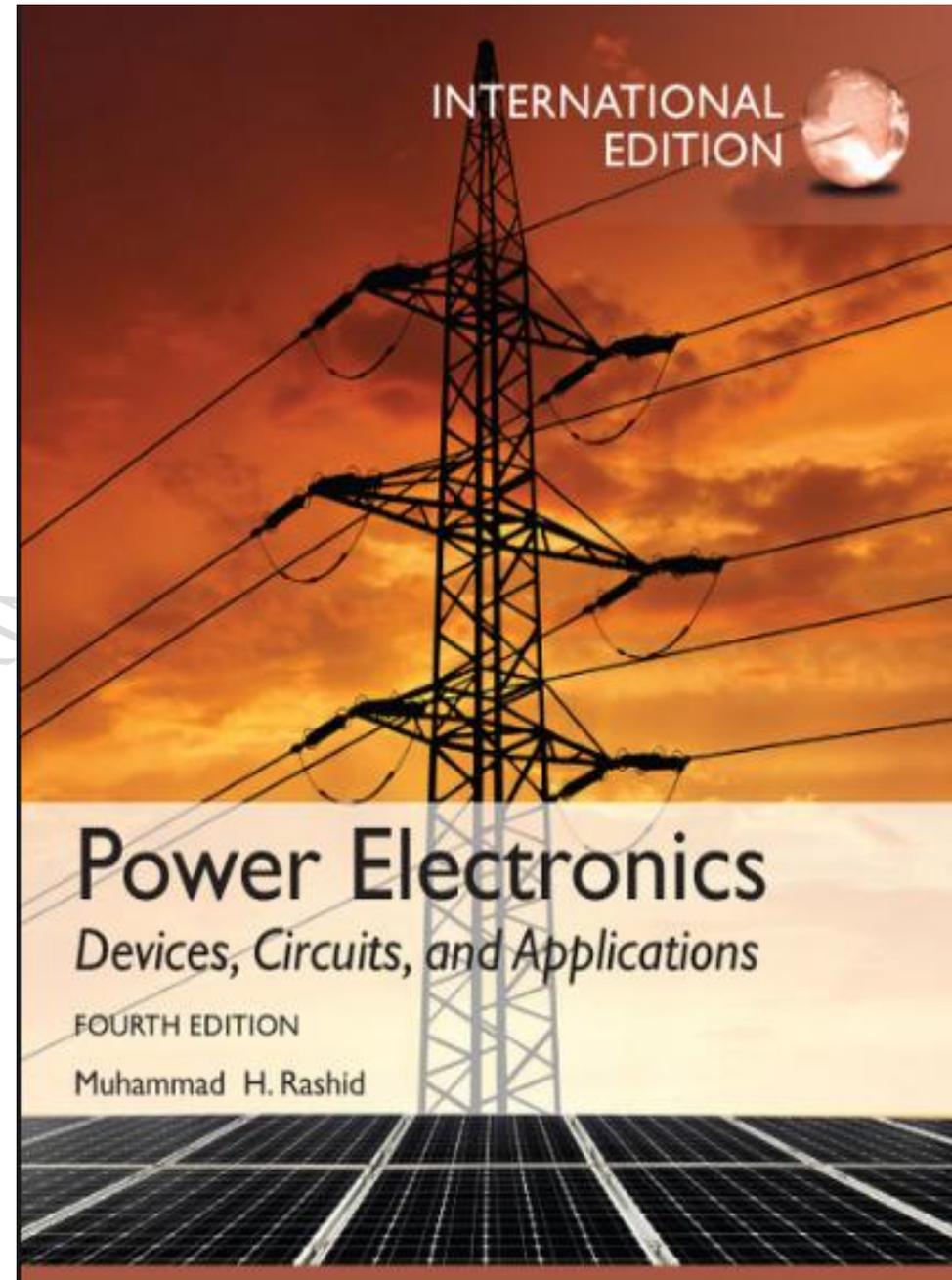Prepared by: Lec. Dr. Mothana Amaar Hassan
Laser and Optoelectronic Engineering
Department



Ref: Power Electronics 4th edition/ Muhammed H. Rashid


Lecture No.8


Three-Phase Diode Rectifiers

There are two types of three-phase diode rectifier, star rectifiers and bridge rectifiers.

Three-Phase Star Rectifiers

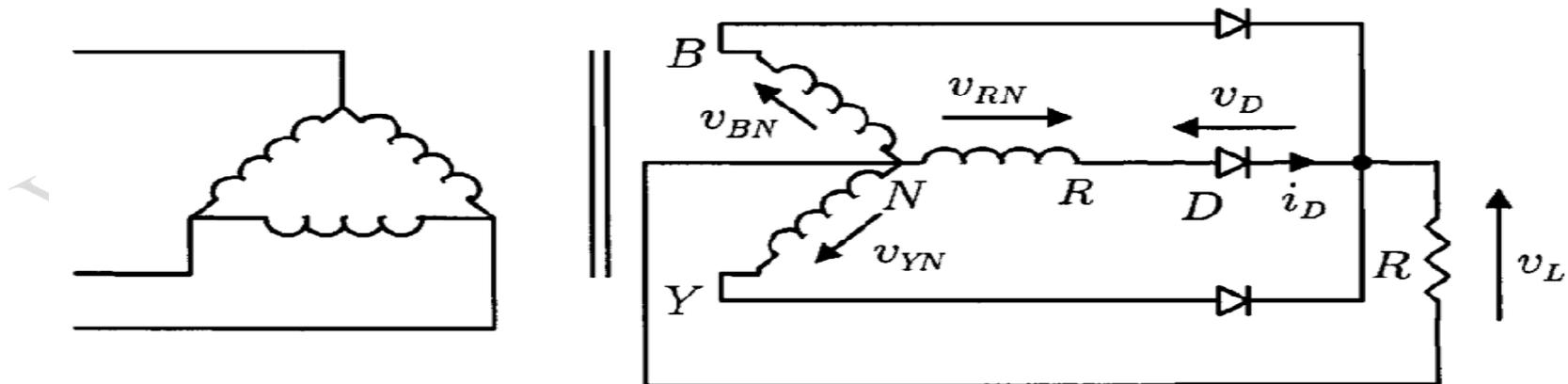A basic three-phase star rectifier circuit is shown in Figure below. This circuit can be considered as three single-phase half-wave rectifiers combined together. Therefore, it is sometimes referred to as a three-phase half-wave rectifier. The diode in a particular phase conducts during the period when the voltage on that phase is higher than that on the other two phases.



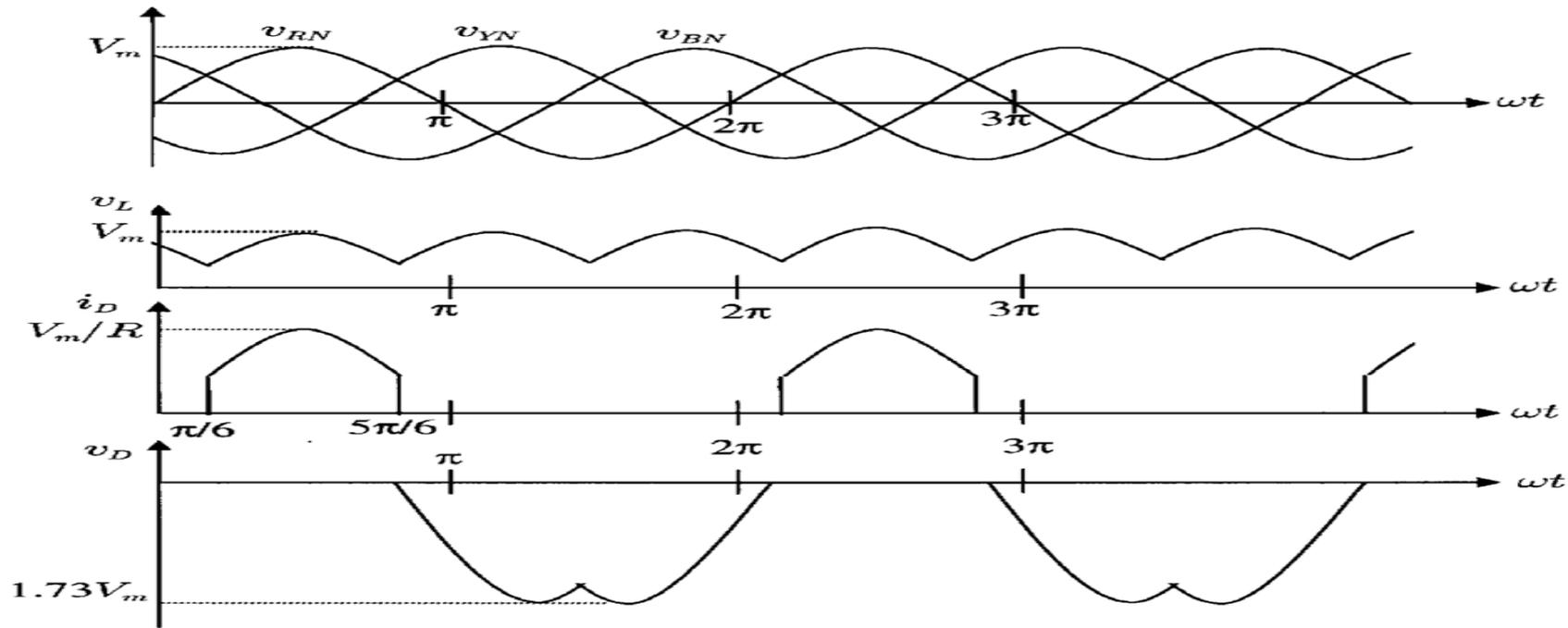

→ It is clear that, unlike the single-phase rectifier circuit, the conduction angle of each diode is $2\pi/3$, instead of π .

→ Taking phase R as an example, diode D conducts from $\pi/6$ to $5\pi/6$.

Therefore, the average value of the output can be found as:

$$V_{dc} = \frac{3}{2\pi} \int_{\pi/6}^{5\pi/6} V_m \sin \theta d\theta$$

Or,

$$V_{dc} = V_m \frac{3}{\pi} \frac{\sqrt{3}}{2} = 0.827 V_m$$

Similarly, the rms value of the output voltage can be found as:

$$V_L = \sqrt{\frac{3}{2\pi} \int_{\pi/6}^{5\pi/6} (V_m \sin \theta)^2 d\theta}$$

Or,

$$V_L = V_m \sqrt{\frac{3}{2\pi} \left(\frac{\pi}{3} + \frac{\sqrt{3}}{4} \right)} = 0.84 V_m$$

The rms current in each transformer secondary winding can also be found as:

$$I_s = I_m \sqrt{\frac{1}{2\pi} \left(\frac{\pi}{3} + \frac{\sqrt{3}}{4} \right)} = 0.485 I_m$$

- It is clear that the peak inverse voltage (PIV) of the diodes is equal to $1.73V_m$ during their blocking state. Hence, the Peak Repetitive Reverse Voltage (V_{RRM}) rating of the diodes must be chosen to be higher than $1.73V_m$ to avoid reverse breakdown.
- During its conducting state, each diode has a forward current that is equal to the load current and, therefore, the Peak Repetitive Forward Current (I_{FRM}) rating of these diodes must be chosen to be higher than the peak load current $I_m = V_m \times R$ in practice.

→ Form factor of diode current $I_s / I_{dc} = 1.76$

→ The rectification ratio is:

$$\frac{P_{dc}}{P_L} = \frac{V_{dc} I_{dc}}{V_L I_L}$$

$$FF = \frac{V_L}{V_{dc}} \quad \text{or} \quad \frac{I_L}{I_{dc}}$$

→ Form factor of three-phase half-wave rectifier

$$FF = \frac{0.84V_m}{0.827V_m} = 1.0165$$


→ Ripple factor of three-phase half-wave rectifier

$$\begin{aligned}\text{RF} &= \sqrt{\left(\frac{V_L}{V_{dc}}\right)^2 - 1} = \sqrt{\text{FF}^2 - 1} \\ &= 0.182\end{aligned}$$

LASER ENGINEERING BRANCH

University of Technology
Laser and Optoelectronic Engineering
Department
Power Electronics/2018-2019)
For the third years (Laser Engineering)

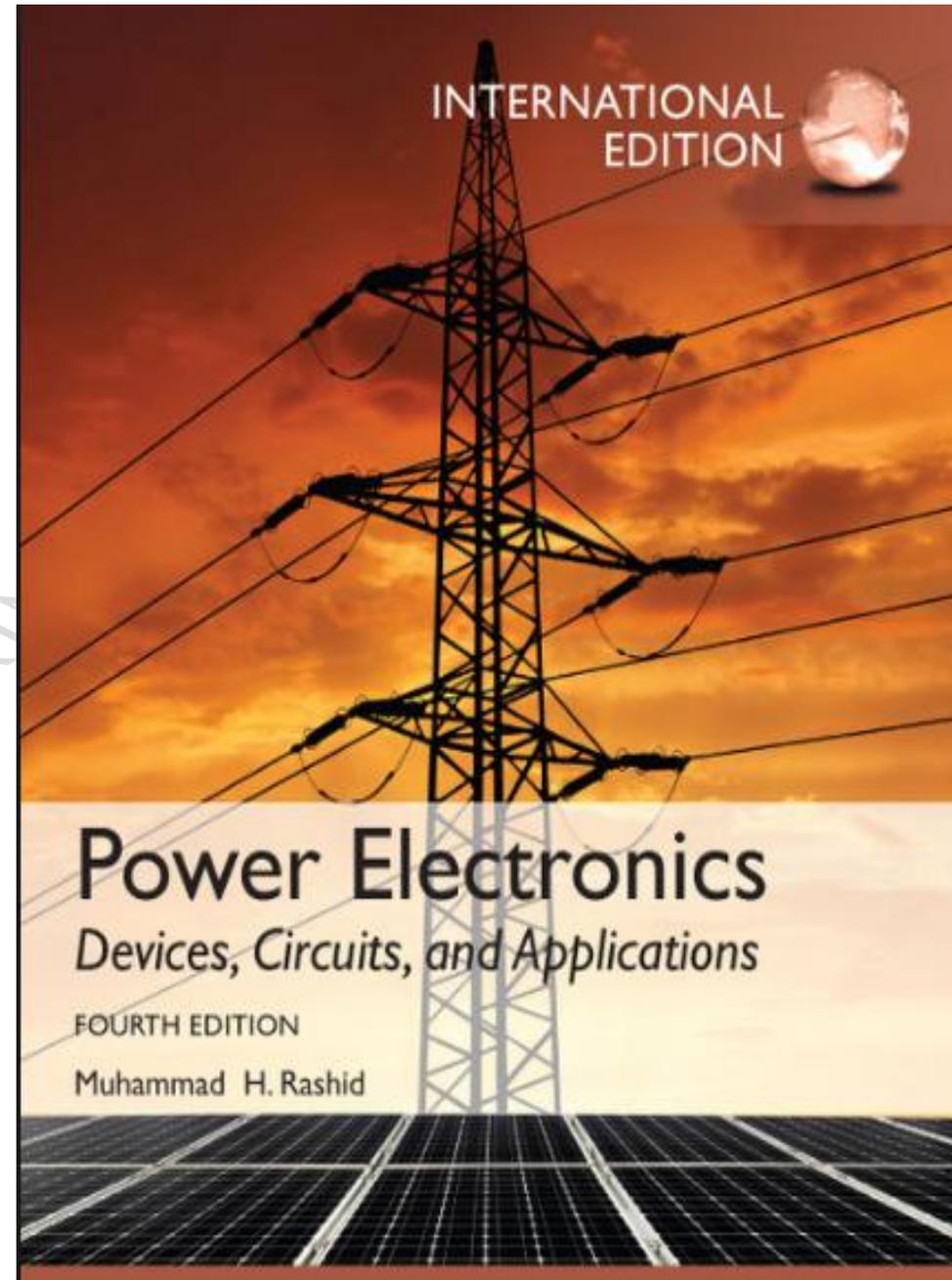Prepared by: Lec. Dr. Mothana Amaar Hassan
Laser and Optoelectronic Engineering
Department




Ref: Power Electronics 4th edition/ Muhammed H. Rashid

Lecture No.9

Three-Phase Bridge Rectifiers

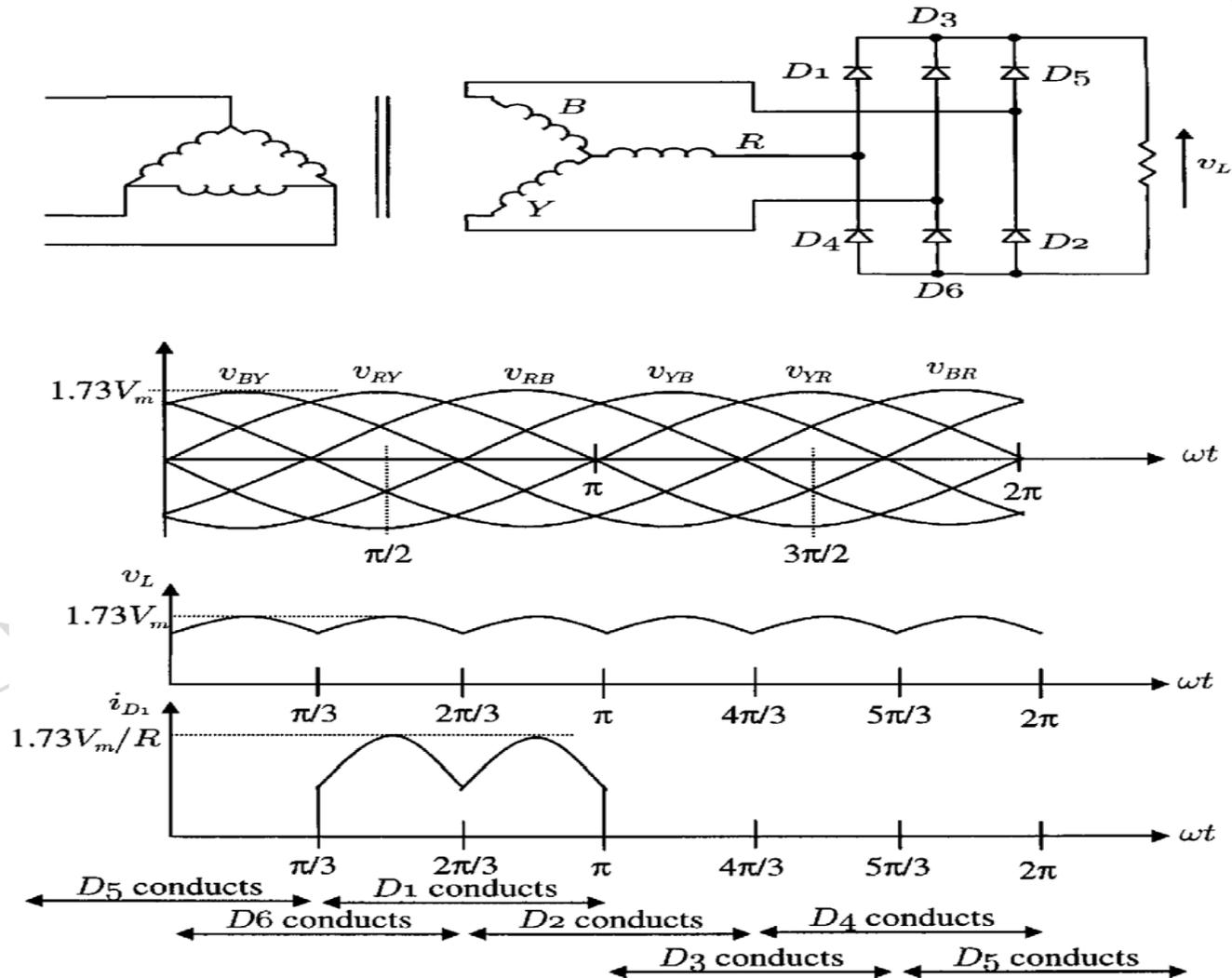Three-phase bridge rectifiers are commonly used for high power applications because they have the highest possible transformer utilization factor for a three-phase system.



The diodes are numbered in the order of conduction sequences and the conduction angle of each diode is $2\pi/3$. The conduction sequence for diodes is **12, 23, 34, 45, 56, and 61**. The line voltage is **1.73** times the phase voltage of a three-phase star-connected source.

The average values of the output can be found as:

$$V_{dc} = \frac{6}{2\pi} \int_{\pi/3}^{2\pi/3} \sqrt{3} V_m \sin \theta d\theta$$

Or,

$$V_{dc} = V_m \frac{3\sqrt{3}}{\pi} = 1.654 V_m$$

Similarly, the rms value of the output voltage can be found as:

$$V_L = \sqrt{\frac{9}{\pi} \int_{\pi/3}^{2\pi/3} (V_m \sin \theta)^2 d\theta}$$

Or,

$$V_L = V_m \sqrt{\frac{3}{2} + \frac{9\sqrt{3}}{4\pi}} = 1.655 V_m$$

The rms current in each transformer secondary winding can also be found as:

$$I_s = I_m \sqrt{\frac{2}{\pi} \left(\frac{\pi}{6} + \frac{\sqrt{3}}{4} \right)} = 0.78 I_m$$

The rms current through a diode is:

$$I_D = I_m \sqrt{\frac{1}{\pi} \left(\frac{\pi}{6} + \frac{\sqrt{3}}{4} \right)} = 0.552 I_m$$


Where, $I_m = 1.73 V_m/R$.

- The dc output voltage is slightly lower than the peak line voltage or 2.34 times the rms phase voltage.
- The Peak Repetitive Reverse Voltage (V_{RRM}) rating of the employed diodes is 1.05 times the dc output voltage.
- The Peak Repetitive Forward Current (I_{FRM}) rating of the employed diodes is 0.579 times the dc output current.

Example 3.4

A three-phase rectifier has a purely resistive load of R. Determine

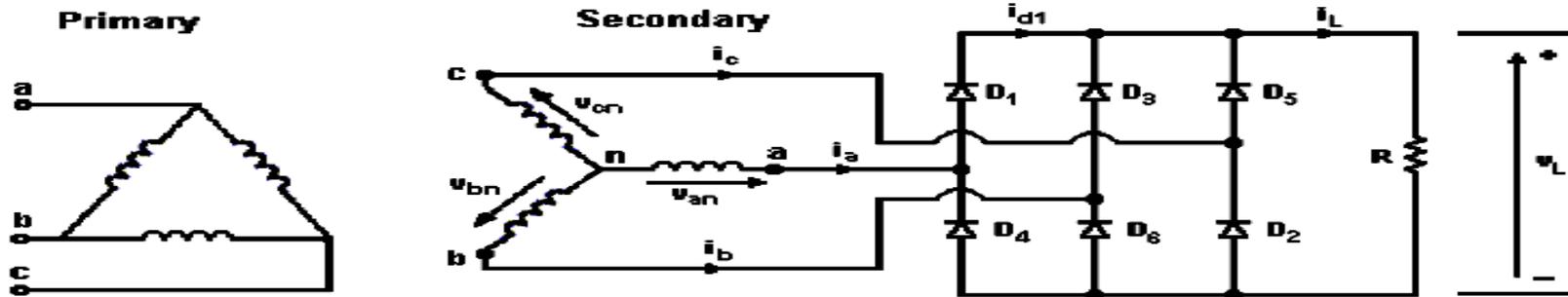- a. The efficiency
- b. The form factor
- c. The rripple factor



Solution

a. Efficiency,

$$\eta = \frac{P_{dc}}{P_L}$$

Now:

$$P_{dc} = V_{dc} \times I_{dc} \quad P_L =$$

Since:

$$V_L \times I_L$$

$$V_{dc} = V_m \frac{3\sqrt{3}}{\pi} = 1.654 V_m$$

$$I_{dc} = \frac{V_{dc}}{R} = \frac{1.654 V_m}{R}$$

$$V_L = V_m \sqrt{\frac{3}{2} + \frac{9\sqrt{3}}{4\pi}} = 1.655 V_m$$

$$I_L = \frac{V_L}{R} = \frac{1.655 V_m}{R}$$

$$\eta = \frac{(1.65 V_m)^2 R}{(1.655 V_m)^2 R} = 99.85\%$$

b. Form factor:

$$FF = \frac{1.655 V_m}{1.654 V_m} = 1.0008$$

c. Ripple factor:

$$RF = \sqrt{\left(\frac{V_L}{V_{dc}}\right)^2 - 1} = \sqrt{FF^2 - 1}$$

$$= 4\%$$

e. V_m = peak line to neutral voltage But $V_{dc} = 1.654 V_m = 280.7 \text{ V}$

$$\Rightarrow V_m = \frac{280.7}{1.654} = 169.7 \text{ V}$$

PIV = peak inverse value of secondary line to line voltage
 $= 169.7 \times 3 = 293.9 \text{ Volt}$

e. The average diode current I_{dc} is given by:

$$I_{dc} = \frac{2 \times 2}{2\pi} \int_0^{\pi/6} I_m \cos \omega t \, d(\omega t)$$

$$I_{dc} = \frac{2I_m}{\pi} \sin\left(\frac{\pi}{3}\right) = 0.318 I_m$$

If the average load current is I_{dc} and each diode is on for 120° of a cycle of 360° then average diode current = $1/3 \times$ average load current

$$I_d = \frac{I_{dc}}{3} = \frac{60}{3} = 20 \text{ A}$$

$$\therefore I_m = \frac{20}{0.318} = 62.83 \text{ A}$$

W.1 The single-phase full wave rectifier has a purely resistive load of R , determine:

a) The efficiency,

b) The ripple factor RF ,

c) The peak inverse voltage PIV of diode NOTE: Drive any formula that used in solution

W.2 The single-phase half wave rectifier has R-L load with $R= 5\Omega$ and $L= 6.5\text{mH}$. The input voltage $V_s=220\text{V}$ at 50Hz , determine:

a) The average diode current

b) The rms diode current

c) The rms output current

d) The average output current

NOTE: Drive any formula that used in solution

H.W3 The single-phase full wave rectifier has a purely resistive load of R , and $I_L=10\text{A}$ and average power = 100Watt , determine:

-The efficiency,

-The form factor and ripple factor,


-The peak inverse voltage PIV of diode, NOTE: Drive any formula that used in solution

H.W4 The diode in the single-phase half wave rectifier has a reverse recovery time of $t_{rr}= 150\mu\text{sec}$ and the source voltage $V_s= 200\text{V}$ at frequency = 5kHz . Calculate the average output voltage.

H.W5: Design the single phase half wave rectifier supply the HeNe laser tube. The voltage across tube is 1.8kV and the current pass through tube is 10mA . The designer has two diodes with $\text{PIV}=1.5\text{kV}$ and saturation current are $I_{s1}=100\mu\text{A}$ and $I_{s2}=120\mu\text{A}$ respectively.

University of Technology
Laser and Optoelectronic Engineering
Department
Power Electronics/2018-2019)
For the third years (Laser Engineering)

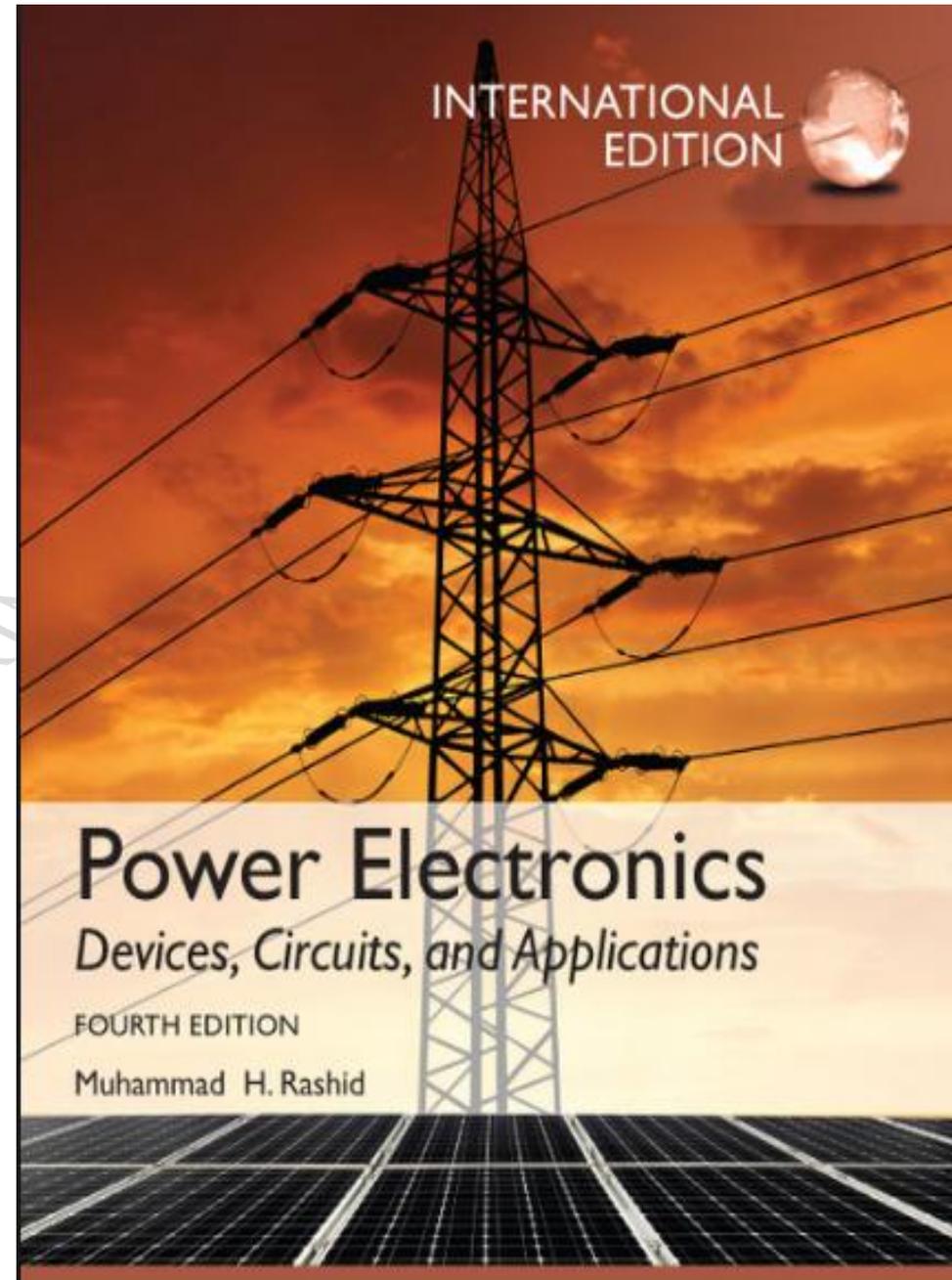Prepared by: Lec. Dr. Mothana Amaar Hassan
Laser and Optoelectronic Engineering
Department



Ref: Power Electronics 4th edition/ Muhammed H. Rashid

Lecture No.1

INTRODUCTION TO POWER ELECTRONICS

Definition

- Power electronics refers to control and conversion of electrical power by power semiconductor devices wherein these devices operate as switches.
- Advent of silicon-controlled rectifiers, abbreviated as SCRs, led to the development of a new area of application called the power electronics.
- Prior to the introduction of SCRs, mercury-arc rectifiers were used for controlling electrical power, but such rectifier circuits were part of industrial electronics and the scope for applications of mercury-arc rectifiers was limited.
- Once the SCRs were available, the application area spread to many fields such as drives, power supplies, aviation electronics & high frequency inverters.

Main Task of Power Electronics

- Power electronics has applications that span the whole field of electrical power systems, with the power range of these applications extending from a few VA/Watts to several MVA / MW.
- The main task of power electronics is to control and convert electrical power from one form to another.
- The four main forms of conversion are:
 - **Rectification referring to conversion of AC voltage to DC voltage,**
 - **DC-to-AC conversion,**
 - **DC-to DC conversion,**
 - **AC-to-AC conversion**

- "Electronic power converter" is the term that is used to refer to a power electronic circuit that converts voltage and current from one form to another.

These converters can be classified as:

- Rectifier converting an ac voltage to a dc voltage,
- Inverter converting a dc voltage to an ac voltage,
- Chopper or a switch-mode power supply that converts a dc voltage to another dc voltage, and
- Cycloconverter converts an ac voltage to another ac voltage.

Rectification

- Rectifiers can be classified as uncontrolled and controlled rectifiers, and the controlled rectifiers can be further divided into semi-controlled and fully controlled rectifiers.
- Uncontrolled rectifier circuits are built with diodes, and fully controlled rectifier circuits are built with SCRs. Both diodes and SCRs are used in semi-controlled rectifier circuits.
- There are several rectifier configurations. The popular rectifier configurations are listed below.
 - Single-phase half wave rectifier,
 - Single-phase full wave rectifier,
 - Single-phase half wave controlled rectifier,
 - Single-phase semi-controlled full wave rectifier,
 - Single-phase fully controlled full wave rectifier,
 - Three-phase half wave rectifier,
 - Three-phase bridge rectifier,
 - Three-phase half wave controlled rectifier,
 - Three-phase semi-controlled bridge rectifier
 - Three-phase fully controlled bridge rectifier
- Power rating of a single-phase rectifier tends to be lower than 10 kW. Three-phase bridge rectifiers are used for delivering higher power output, up to 500 kW at 500 V dc or even more.
- There are many applications for rectifiers. Some of them are:
 - Variable speed dc drives,
 - Battery chargers,
 - DC power supplies and Power supply for a specific application like electroplating

DC-to-AC Conversion

- The converter that changes a dc voltage to an alternating voltage is called an inverter.
- Earlier inverters were built with SCRs.
- Since the circuitry required turning the SCR off tends to be complex, other power semiconductor devices such as bipolar junction transistors, power MOSFETs, insulated gate bipolar transistors (IGBT) and MOS- controlled thyristors (MCTs) are used nowadays.
- Some of the applications of an inverter are listed below:
 - Emergency lighting systems,
 - AC variable speed drives,

- Uninterrupted power supplies,
- Frequency converters

DC-to-DC Conversion

- A SCR, power BJT or a power MOSFET is normally used in such a converter and this converter is called a switch-mode power supply.
- A switch-mode power supply can be of one of the types listed below:
 - Step-down switch-mode power supply,
 - Step-up switch-mode power supply,
 - Fly-back converter,
 - Resonant converter
- The typical applications for a switch-mode power supply or a chopper are:
 - DC drive
 - Battery charger
 - DC power supply

AC-to-AC Conversion

- A cycloconverter converts an ac voltage, such as the mains supply, to another ac voltage.
- The amplitude and the frequency of input voltage to a cycloconverter tend to be fixed values, whereas both the amplitude and the frequency of output voltage of a cycloconverter tend to be variable.
- A typical application of a cycloconverter is to use it for controlling the speed of AC traction motor and most of these cycloconverters have a high power output, of the order a few megawatts and SCRs are used in these circuits.


Power electronic devices (part I)

1. The power diode


Diode Approximations

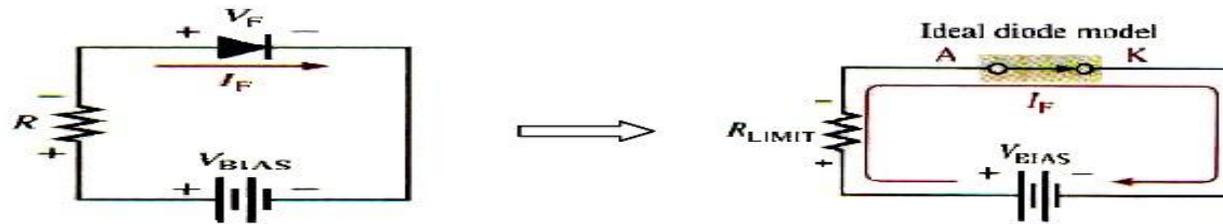i. The Ideal Model


- Think it as switch
- When forward biased, act as a closed (ON) switch
- When reverse biased, act as open (off) switch



Ideal diode model for forward bias

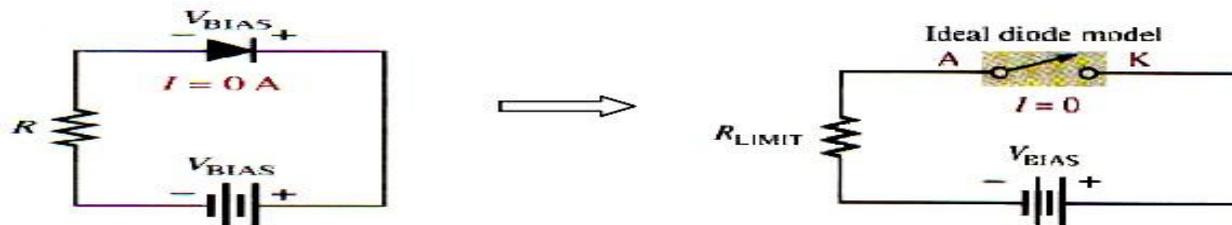

Ideal diode model for reverse bias



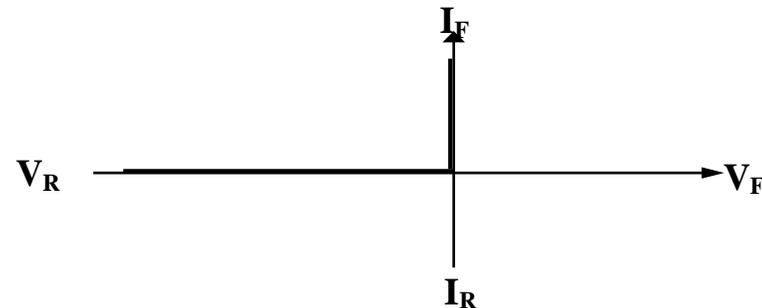


Ideal Characteristic curve (blue) for Ideal model

- This model neglects the effect of the barrier potential, the internal resistance, and other parameters.

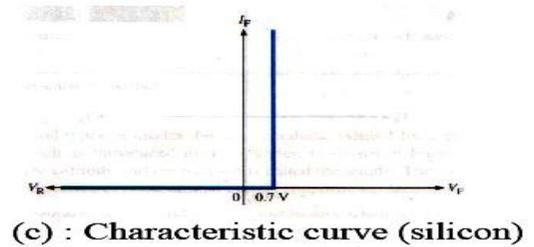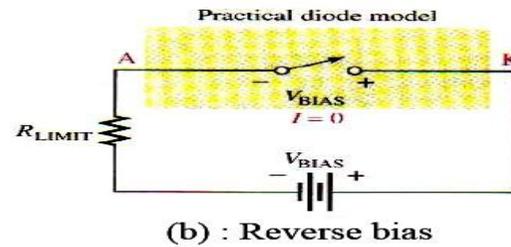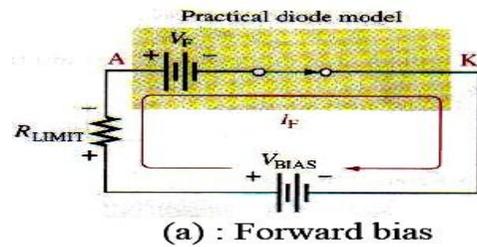ii. The Barrier Potential Model



- The forward biased diode is represented as a closed switch in series with a small ‘battery’ equal to the barrier potential V_B (0.7 V for Si and 0.3 V for Ge)
- The positive end of the equivalent battery is toward the anode.
- This barrier potential cannot be measured by using a multimeter, but it has the effect of a battery when forward bias is applied.
- The reverse biased diode is represented by an open switch, because barrier potential does not affect reverse bias.




The practical model of a diode

The Complete Diode Model

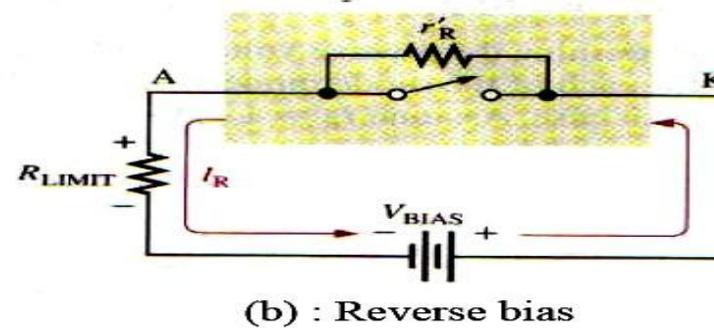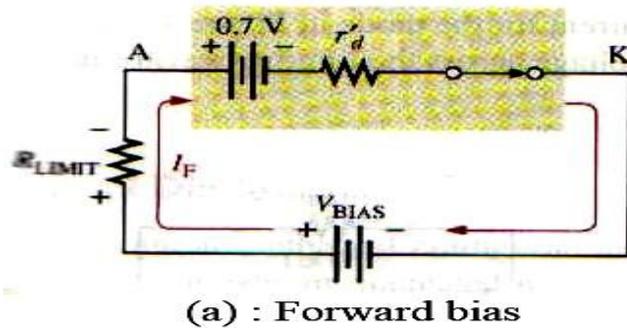- More accurate
- The forward biased diode model with both the barrier potential and low forward (bulk) resistance (r'_d)



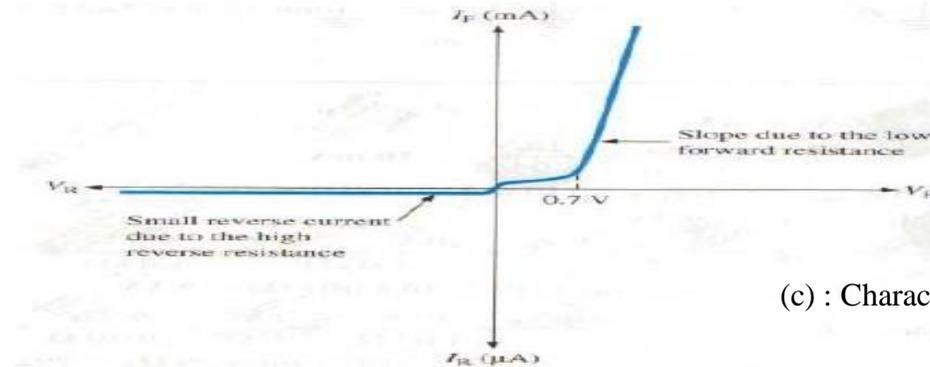

(c) : Characteristic curve (silicon)

Diode Characteristics

- A power diode is a two terminal pn – junction device.
- The magnitude of this voltage drop depends on:
 - a) on the manufacturing process
 - b) junction temperature
- When the cathode potential is positive with respect to the anode:
 - ⇒ The diode is said to be reverse biased
 - ⇒ A small reverse current (also known as leakage current) in the range of micro or miliampere, flows through it.
 - ⇒ It increases slowly in magnitude with the reverse voltage until the avalanche or zener voltage is reached.
- The $v - I$ characteristics shown above can be expressed by an equation known as ‘Schockley diode equation’ and it is given under dc steady state operation by:

$$I_D = I_S \left(e^{V_D / nV_T} - 1 \right)$$

- Where:

I_D = Current through the diode, A

V_D = Diode voltage (forward voltage)

I_S = Leakage current (or reverse saturation). n = emission coefficient

V_T = Thermal Voltage

$$V_T = \frac{kT}{q}$$

q = electron charge : 1.6022×10^{-19} C T = absolute temperature in Kelvin

k = Boltzman's constant : 1.3806×10^{-23} J / K

• The diode characteristics can be divided into three region:

1. Forward – biased region, where $V_D > 0$
2. Reverse – biased region, where $V_D < 0$
3. Breakdown region, where $V_D < -V_{BR}$

Forward – biased region

- $V_D > 0$
- Diode current I_D very small if V_D is less than a specific value V_T (0.7V)
- Diode conducts fully if V_D is higher than this value V_T , which is referred to as the threshold voltage or the turn-on voltage
- The threshold voltage is a voltage at which the diode conducts fully.

Reverse – biased region

- $V_D < 0$
- If V_D is negative and $|V_D| \gg V_T$, which occurs for $V_D < -0.1$, the exponential term in Shockley equation becomes negligibly small compared to unity and the diode current I_D becomes:

$$I_D = I_S (e^{V_D / nV_T} - 1) \cong -I_S$$

Breakdown region

- Reverse voltage is high.
- Magnitude of reverse voltage exceeds a specified voltage known as the breakdown voltage, V_{BR}
- I_R increases rapidly with a small change in reverse voltage beyond V_{BR} .
- The operation in this region will not be destructive provided that the power dissipation is within a 'safe level' that is specified in the manufacture's data sheet.
- But it has to limit I_R in order to limit the power dissipation within a permissible value

Home work :

The forward voltage drop of a power diode is $V_D = 1.2$ V at $I_D = 300$

A. Assuming that $n = 2$ and $V_T = 25.7$ mV, find the reverse saturation current I_S .